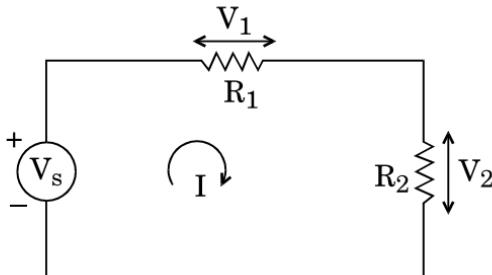


**BACHELOR OF SCIENCE (B.Sc.)****Term-End Examination****June, 2021****PHYSICS****PHE-10 : ELECTRICAL CIRCUITS AND ELECTRONICS***Time : 2 hours**Maximum Marks : 50*

**Note :** All questions are **compulsory**. However, internal choices are given. Use of calculator is allowed. Symbols have their usual meanings.

**1.** Attempt any **five** parts :  $5 \times 2 = 10$

- (a) Write the expression for  $V_1$  in the following circuit.



- (b) Write any two processes responsible for charge carrier transport in semiconductors.

(c) A multistage amplifier consists of three stages. The voltage gains of the stages are 30, 40 and 50. What will be the overall gain of the amplifier ?

(d) Fill in the blanks :

In an op-amp IC 741, the input pins are numbered \_\_\_\_\_ and \_\_\_\_\_ while output pin is numbered \_\_\_\_\_ .

(e) Write the decimal equivalent of  $136_{16}$  hex number.

(f) Are the following characteristics of LM 380 *True* or *False* :

- (i) It can work on a wide range of supply voltage from 5 to 22 V.
- (ii) It has internally fixed gain of 100.


(g) Draw the symbol of logic gate for truth table given below and write its name.

A	B	Y
1	1	0
0	0	1
1	0	0
0	1	0

2. Attempt any ***two*** parts :  $2 \times 5 = 10$

(a) State and prove Thevenin's theorem. 5

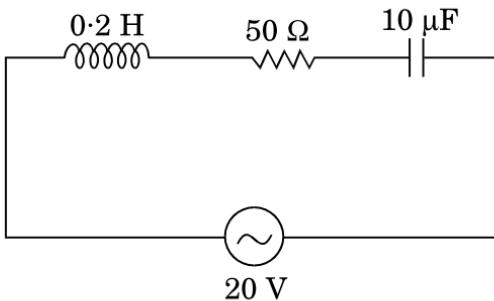(b) For the circuit given below, find the resonant frequency and Q-factor of the circuit. Will the value of Q be different if applied voltage changes from 20 V to 25 V ?  $2+2+1$



(c) Draw the circuit diagram of a common emitter configuration of npn-BJT. Plot its input and output characteristic curves.  $2+1+2$

3. Attempt any ***two*** parts :  $2 \times 5 = 10$

(a) Define h-parameters of a four terminal black box in terms of partial derivatives of currents and voltages. Write the expression of current gain for a CE amplifier in terms of h-parameters. 4+1

(b) Draw the block diagram of a basic Wien Bridge Oscillator using identical resistors of  $220 \text{ k}\Omega$  and capacitors of  $250 \text{ pF}$ . Calculate its frequency of oscillations.  $3+2$

(c) Define Ripple Factor and Rectification Efficiency of a rectifier. Explain the working of a capacitance filter used with a full wave rectifier.

2+3

4. Attempt any ***two*** parts :  $2 \times 5 = 10$

(a) (i) Give values of the following characteristics of an ideal op-amp :

Voltage gain, Input resistance, Output resistance, CMRR, Slew Rate and Band width.

(ii) Draw the circuit of voltage level detector using an op-amp.

3+2

(b) Draw the circuit diagram of a basic integrator using op-amp 741. Plot outputs of the integrator if the inputs are

(i) Sine wave, and

(ii) Square wave.

3+2

(c) Draw the circuit of an audio power amplifier with variable gain up to 50 using IC LM 380.

5

5. Attempt any ***two*** parts :

$2 \times 5 = 10$

(a) (i) Draw the circuits for realisation of AND gate using diodes and NOT gate using a transistor.

(ii) Write the truth table for

$$Y = AB + A(\bar{B} + C).$$

3+2

(b) A 5-bit DAC produces an 11 mV output for a digital input of 10110. What will  $V_{out}$  be for a digital input of 11100 ?

5

(c) With the help of a diagram, explain the functioning of a basic function generator.

5

\_\_\_\_\_

## विज्ञान स्नातक (बी.एस सी.)

### सत्रांत परीक्षा

जून, 2021

### भौतिक विज्ञान

पी.एच.ई.-10 : विद्युत् परिपथ और इलेक्ट्रॉनिकी


समय : 2 घण्टे

अधिकतम अंक : 50

**नोट:** सभी प्रश्न अनिवार्य हैं। तथापि, आंतरिक विकल्प दिए गए हैं। कैल्कुलेटर का प्रयोग करने की अनुमति है। प्रतीकों के अपने सामान्य अर्थ हैं।

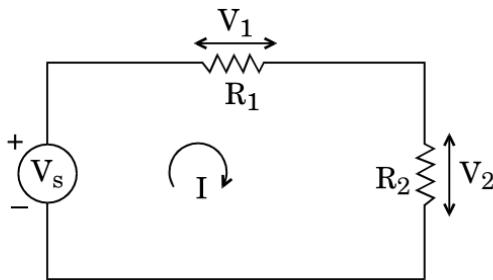1. किन्हीं पाँच भागों को हल कीजिए :  $5 \times 2 = 10$

(क) निम्नलिखित परिपथ में  $V_1$  का व्यंजक लिखिए।



(ख) अर्धचालकों में आवेश वाहकों के अभिगमन के लिए उत्तरदायी कोई दो प्रक्रम लिखिए।

(ग) एक बहुपदी प्रवर्धक के तीन पद हैं। इन पदों की वोल्टता लब्धियाँ 30, 40 और 50 हैं। प्रवर्धक की समग्र लब्धि कितनी होगी ?

(घ) रिक्त स्थान भरिए :

IC 741 ऑप-एम्प में निवेश टर्मिनलों के पिनों के नंबर \_\_\_\_\_ और \_\_\_\_\_ होते हैं और निर्गम टर्मिनल के पिन का नंबर \_\_\_\_\_ होता है।

(ङ) षोडशाधारी संख्या  $136_{16}$  का दशमलव तुल्य लिखिए।

(च) बताइए कि LM 380 के निम्नलिखित अभिलक्षणिक सत्य हैं या असत्य :

(i) यह 5 से 22 V की वोल्टता सप्लाई के विस्तृत परास में काम कर सकता है।

(ii) इसकी आन्तरिक स्थिर लब्धि 100 है।

(छ) निम्नलिखित सत्यमान सारणी के लिए संगत तर्क गेट का नाम लिखिए और इसका प्रतीक खींचिए।

A	B	Y
1	1	0
0	0	1
1	0	0
0	1	0

2. किन्हीं दो भागों को हल कीजिए :


$2 \times 5 = 10$

(क) थेवेनिन प्रमेय का कथन लिखिए और इसे सिद्ध कीजिए।

5

(ख) नीचे दिए गए परिपथ की अनुनादी आवृत्ति और Q-गुणांक परिकलित कीजिए। यदि अनुप्रयुक्त वोल्टता को 20 V से 25 V तक बढ़ाया जाए, तो क्या Q-गुणांक के मान में परिवर्तन होगा ?

2+2+1

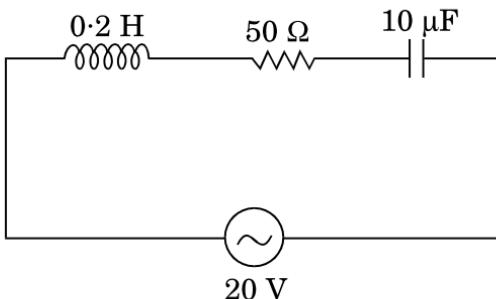

(ग) npn ट्रान्जिस्टर (BJT) के सर्वनिष्ठ उत्सर्जक (CE) विन्यास का परिपथ चित्र खींचिए। इसके निवेश और निर्गम अभिलक्षणिक वक्र खींचिए।

2+1+2

3. किन्हीं दो भागों को हल कीजिए :

$2 \times 5 = 10$

(क) चार टर्मिनल वाले काले बॉक्स के h-प्राचलों को धाराओं और वोल्टताओं के आंशिक अवकलजों के पदों में परिभाषित कीजिए। CE प्रवर्धक की धारा लिधि का व्यंजक h-प्राचलों के पदों में लिखिए।

4+1

(ख) आधारभूत बीन सेतु दोलित्र का ब्लॉक आरेख खींचिए जिसमें समान प्रतिरोध  $220\text{ k}\Omega$  के प्रतिरोधक और समान धारिता  $250\text{ pF}$  के संधारित्र लगे हों। इसके दोलनों की आवृत्ति परिकलित कीजिए।

3+2

(ग) दिष्टकारी के ऊर्मिका गुणक और दिष्टकरण दक्षता को परिभाषित कीजिए। पूर्ण तरंग दिष्टकारी के साथ जुड़े धारिता निस्यन्दक की कार्यप्रणाली समझाइए। 2+3

4. किन्हीं दो भागों को हल कीजिए :  $2 \times 5 = 10$

(क) (i) एक आदर्श ऑप-एम्प के लिए निम्नलिखित अभिलक्षणों के मान बताइए :  
वोल्टता लब्धि, निवेश प्रतिरोध, निर्गम प्रतिरोध,  
CMRR, द्रुत घूर्णन दर और बैंड चौड़ाई।

(ii) ऑप-एम्प का उपयोग करके एक वोल्टता स्तर संसूचक का परिपथ चित्र खींचिए। 3+2

(ख) ऑप-एम्प 741 का उपयोग करके एक बुनियादी समाकलक का परिपथ चित्र खींचिए। (i) ज्या तरंग, और (ii) वर्ग तरंग निवेशों के लिए समाकलक के निर्गम तरंगरूप खींचिए। 3+2

(ग) IC LM 380 का उपयोग करके 50 तक की परिवर्ती लब्धि वाले श्रव्य शक्ति प्रवर्धक का परिपथ चित्र खींचिए। 5

5. किन्हीं दो भागों को हल कीजिए :

$2 \times 5 = 10$

(क) (i) डायोडों के प्रयोग से बने AND गेट और ट्रांजिस्टर की सहायता से बने NOT गेट के परिपथ चित्र खींचिए ।

(ii)  $Y = AB + A(\bar{B} + C)$  की सत्यमान सारणी लिखिए ।

3+2

(ख) एक 5-बिट DAC 10110 अंकीय निवेश के लिए 11 mV का निर्गत उत्पन्न करता है । 111000 अंकीय निवेश के लिए  $V_{out}$  क्या होगा ?

5

(ग) आरेख की सहायता से मूल फलन जनित्र की कार्यप्रणाली समझाइए ।

5

\_\_\_\_\_