

00835

B.Sc. (NAUTICAL SCIENCE)

Term-End Examination

June, 2015

BNA-013 : ELECTRICITY AND ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Attempt *three* questions from each section.
Questions no. 1 and 5 are **compulsory**.
Non-programmable scientific calculator is allowed.

SECTION A

(Electricity)

1. (a) Explain Kirchhoff's current and voltage laws with one example. 10
- (b) Explain the limitations of Ohm's law. 5
2. (a) Define the following terms and also give formula : $4 \times 1 \frac{1}{2} = 6$
- (i) Voltage
 - (ii) Electrical Power
 - (iii) Electrical Energy
 - (iv) Power Factor
- (b) Explain the effect of temperature on the resistance of metallic conductor. 4

3. (a) Explain Biot-Savart law. 5
- (b) Define capacitance and explain how equivalent capacitance is calculated when two capacitors are connected in parallel. 5
4. (a) Define time period, frequency, amplitude, average and rms value of A.C. 5
- (b) Calculate the highest speed at which the alternator (A.C. generator) can be operated for
- (i) 50 Hz,
- (ii) 60 Hz.
- Consider number of poles 2. 5

SECTION B

(Electronics)

5. (a) Explain the working principle of Radar with a neat sketch and also explain how to find range to target. 10
- (b) Draw the block diagram of superheterodyne receiver and explain about it. 5
6. (a) What are the different types of wave propagation ? Explain any one of them. $2+3=5$
- (b) What is Antenna ? Explain Yagi antenna with a neat sketch. 5
7. (a) How are damped oscillations produced in tank circuit ? 5
- (b) Explain AM diode detector with neat circuit diagram. 5
8. (a) Write short notes on the following : 5
- (i) 7 segment display
- (ii) Light dependent resistor
- (b) Draw neat sketches of transistor in
- (i) Common emitter configuration
- (ii) Common base configuration 5
-