

**B.Tech. Civil (Construction Management)/
B.Tech. Civil (Water Resources Engineering)**

00030 **Term-End Examination**
June, 2015

**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours

Maximum Marks : 70

Note : Answer any five questions in all.

1. (a) Explain the working principle of a transformer and calculate the r.m.s. value of the induced e.m.f. in the secondary winding of a transformer, when a sinusoidal flux 0.2 Wb (max.) links with 55 turns of a transformer secondary winding working at 50 Hz a.c. supply. 6

- (b) What do you understand by 'armature reaction' ? What is the effect of armature reaction in d.c. generator ? 6

- (c) Mention the relative advantages and disadvantages of using a digital indicating instrument over an analog instrument. 2

2. (a) What are interpoles ? What is their function ?
Where are they placed in d.c. machine ? 6
- (b) A 200 kVA, 3300/240 volts, 50 Hz single
phase transformer has 80 turns on the
secondary winding. Assuming an ideal
transformer, calculate : 6
- (i) primary and secondary current on full
load
- (ii) the maximum value of flux
- (iii) the number of primary turns.
- (c) Draw the torque – slip characteristics of a
3-phase induction motor. 2
3. (a) What are the basic components used in
electrical installations ? State briefly the
function of each component. 6
- (b) Explain the necessity for power factor
correction. What are the different methods of
power factor correction ? 6
- (c) When are two 2-terminal networks said to be
equivalent ? 2
4. (a) Discuss how a transistor behaves as an
amplifier. 6
- (b) What are the different types of instructions
available in 8085 microprocessor instruction
set ? 6
- (c) Draw the basic circuit diagram of a
non-inverting op-amp. 2

5. (a) Draw the different kinds of logic gates used in digital circuits. 6
- (b) Explain the working of a dual slope integrating type ADC. 6
- (c) Find the decimal equivalent of $(101011)_2$. 2
6. (a) What is a multiplexer ? Draw the symbol of a 4-to-1 multiplexer showing various inputs and outputs and write its truth table. 6
- (b) Design a summing amplifier circuit using an operational amplifier to obtain an output voltage V_o given by $0.1 V_{i1} - 10 V_{i2} - 102 V_{i3}$ where V_{i1} , V_{i2} and V_{i3} are input voltages. 4
- (c) Design a Wein Bridge Oscillator for a frequency of 100 kHz. 4
7. (a) For an 8085 microprocessor : 8
- (i) What does the signal IO/\overline{M} signify and how is it normally used ?
- (ii) What is the function of stack pointer ?
- (b) What is meant by an interrupt in a microprocessor ? List all the interrupts that are available in 8085 microprocessor. 6