

**B.Tech. - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**00706 June, 2015**

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS  
DESIGN**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any seven questions. All questions carry equal marks.*

---

1. (a) Draw the schematic symbol and block diagram of an operational amplifier and explain each block. 5
- (b) Define Input offset voltage and current, Input voltage range, CMRR and Slew rate. 5
  
2. Explain the various open-loop opamp configurations and also derive the expressions for output voltage of each configuration for ideal case. 10

3. (a) Explain voltage follower. Why is it also called non-inverting buffer? 5
- (b) Explain difference amplifier, and its limitations in precision differential measurements. 5
4. (a) Explain the difference between Clipper and Clamper circuits. 5
- (b) What is the difference between basic comparator and schmitt trigger? Also list the limitations of OP-AMP as comparator. 5
5. What is the name of the circuit that is used to detect the peak value of non-sinusoidal input waveforms? Explain its complete operation with suitable diagram. 10
6. Explain V to F and F to V converters with neat diagram and describe its applications. 10
7. Draw the schematic diagram of triangular wave generator using a square wave generator and an integrator. Also draw its input and output waveforms. 10
8. Define a filter. Discuss the various filter types by defining proper transfer functions for each. List the advantages of active filters. 10

9. Write short notes on any *two* of the following :  $2 \times 5 = 10$

- (a) Virtual Short and Virtual Ground
  - (b) Monolithic Timers
  - (c) Log Antilog Amplifiers
-