

**B. Tech. MECHANICAL ENGINEERING
(COMPUTER INTEGRATED
MANUFACTURING) /
B.Tech. (AEROSPACE ENGINEERING) (BTAE)
Term-End Examination
June, 2015**

00303

**BME-021 : PRINCIPLES OF ELECTRICAL AND
ELECTRONICS SCIENCE**

Time : 3 hours

Maximum Marks : 70

Note : Answer any seven questions in all — three questions from Section A, three questions from Section B. Question one is compulsory.

1. State whether the following assertions are *True* or *False*. *10 × 1 = 10*
- (a) Leakage flux exists only in primary circuit of a transformer.
 - (b) Speed control of a 3-phase induction motor by stator voltage control is possible, if load torque increases with speed.
 - (c) In a 3-phase delta connection, line current is equal to $\sqrt{3}$ times the phase current.

- (d) Average value of a sinusoidal ac is slightly greater than its rms value.
- (e) At series resonance, the current is maximum.
- (f) In pure inductive circuit, actual power is infinite.
- (g) Thevenin's theorem is true for both ac and dc circuits.
- (h) Op-Amp 741 can be used as a microprocessor.
- (i) NAND gate can be used as an amplifier.
- (j) Diode is a three terminal device.

SECTION A

Attempt any **three** questions from this section.

2. (a) State and explain Thevenin's theorem with a suitable example. 4
- (b) Find the current in R_1 of the network shown in Figure 1. 6

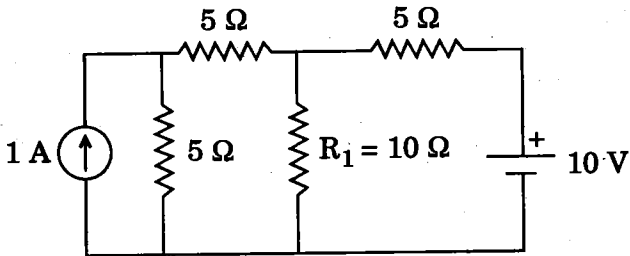


Figure 1

3. (a) For the output waveform of a half-wave rectifier shown in Figure 2, determine (i) rms value, (ii) average value, (iii) form factor. 6

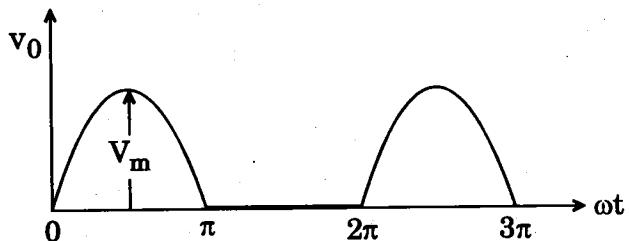


Figure 2

- (b) Draw and explain resonance curve in series RLC circuit. 4

4. (a) Derive the relationship between flux, reluctance and magnetic field intensity of a typical magnetic circuit. 4
- (b) A cast steel magnetic structure made of a bar of cross-section 4 cm^2 is shown in Figure 3. Find the current that the 500 turn magnetizing coil on the left limb should carry so that a flux of 2 mWb is produced in the right limb. Iron has μ as 600. 6

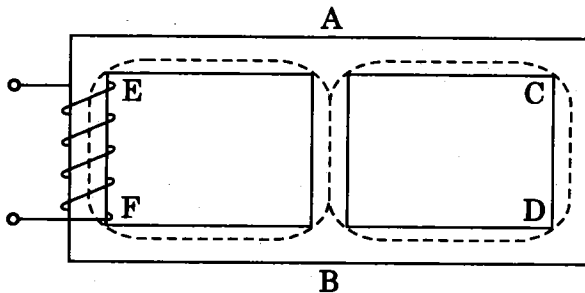


Figure 3

5. (a) Name any three methods of starting a three phase squirrel cage induction motor. Briefly explain any one method. 4
- (b) What is servo motor ? How does a dc servo motor differ from a conventional dc motor ? 3
- (c) A 3- ϕ . 50 Hz, 6-pole induction motor rotates at a speed of 950 rpm. Calculate % slip and frequency of rotor induced emf. 3
6. (a) Explain the concept of power in ac circuits. Draw power triangle and explain it. 4
- (b) If a coil of 150 turns is linked with a flux of 0.01 Wb when carrying a current of 10 amp, calculate the inductance of the coil. 6

SECTION B

Attempt any **three** questions from this section.

7. (a) Give the architecture of 8085 microprocessor. Explain the different buses and registers. 5
- (b) Explain stack pointer, program counter and flags in 8085. 5
8. (a) Draw and explain the electronic circuit of a common emitter amplifier using BJT. 5
- (b) Explain the working of an inverting integrator using op-amp. 5
9. (a) Describe a typical S-R flip-flop. Explain its working principle. 5
- (b) Draw and explain a 3-element shift register using D flip-flop. 5
10. (a) Explain the use of 555 timer as astable multivibrator. 5
- (b) Draw and explain a 6-bit binary weighted DAC. 5
11. (a) Draw the switch configuration, truth table and symbol of a tri-state inverter. 5
- (b) Explain the following instructions : 5
- (i) LDAX
 - (ii) SUI
 - (iii) CMA
-