

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

Term-End Examination

00386

June, 2015

BIELE-005 : INDUSTRIAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : *Question no. 1 is compulsory. Attempt any four questions from the rest. Missing data may be assumed suitably. Use of scientific calculator is permitted. All questions carry equal marks.*

1. Choose the correct answer :

7×2=14

(a) When a UJT is used for triggering an SCR, the shape of the waveform of the voltage obtained from the UJT circuit is

- (i) Sine wave
- (ii) Saw tooth wave
- (iii) Square wave
- (iv) None of the above

(b) The turn-off time of a transistor is

- (i) $t_{OFF} = t_d + t_f$
- (ii) $t_{OFF} = t_s + t_f$
- (iii) $t_{OFF} = t_d + t_r$
- (iv) $t_{OFF} = t_d + t_s$

- (c) A freewheeling diode is used in a controlled rectifier circuit in the case of
- (i) a resistive load
 - (ii) an inductive load
 - (iii) a capacitive load
 - (iv) All the above
- (d) In a single-phase full converter, for continuous conduction each pair of SCRs conduct for
- (i) $\pi - \alpha$
 - (ii) π
 - (iii) α
 - (iv) $\alpha - \pi$
- (e) An ideal transistor switch has
- (i) zero ON-value resistance
 - (ii) infinite OFF-value resistance
 - (iii) no power loss
 - (iv) None of the above
- (f) In a three-phase full wave fully controlled bridge rectifier each SCR conducts for a duration of
- (i) 120°
 - (ii) 60°
 - (iii) 45°
 - (iv) 180°

(g) In a UJT, with V_{BB} as the voltage across two base terminals, the emitter potential at peak point is given by

(i) ηV_{BB}

(ii) ηV_D

(iii) $\eta V_{BB} + V_D$

(iv) $\eta V_D + V_{BB}$

2. (a) Define latching and holding currents as applicable to an SCR. Show these currents on the static volt-ampere characteristic curve of an SCR. 7

(b) Explain the different methods for turning on of an SCR. 7

3. (a) Why is a separate freewheeling diode not needed in the case of a single-phase full wave, half controlled bridge rectifier ? 7

(b) Explain the construction and draw the V-I characteristic curve of a Triac. 7

4. (a) A unijunction transistor used for triggering the silicon controlled rectifier has $R_{B1} = 4 \text{ k}\Omega$ and $R_{B2} = 2.5 \text{ k}\Omega$. Find
(i) the value of intrinsic stand-off ratio.
(ii) Peak point voltage, if $V_{BB} = 15 \text{ V}$ and barrier potential = 0.7 V. 7

(b) Explain the working of an oscillator employing UJT for triggering the SCR. 7

5. Explain how can the transistor can be used as a switching element, with the help of its output characteristic curve for a switching transistor. Also compare the transistor and SCR as switching elements. 14
6. (a) Explain the principle of operation of IGBT. What are its advantages over the power transistors? 7
- (b) Differentiate between full controlled bridge rectifiers and half controlled bridge rectifiers. 7
7. Write short notes on any *two* of the following : $2 \times 7 = 14$
- (a) Three-phase half-wave Delta-Wye rectifier
- (b) dv/dt triggering
- (c) MOS controlled Thyristor
-