

**DIPLOMA IN ELECTRICAL ENGINEERING  
(DELVI)**

**Term-End Examination**

**June, 2015**

00696

**BIEE-033 : ELECTRICAL CIRCUIT THEORY**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions. All questions carry equal marks. Use of scientific calculator is allowed. Assume missing data, if any.*


---

---

1. (a) (i) Current through a load changes linearly with the applied voltage. State the law pertaining to this situation. 2
- (ii) A current of  $3te^{-100t}$  flows through a load on application of supply voltage of  $(0.006 - 0.6t) e^{-100t}$  volts. What power is being absorbed by the load at the time  $t = 5$  ms ? 5
- (b) (i) Define Kirchhoff's voltage law, using mathematical expressions and circuit diagrams. 2

- (ii) Resistors were connected together to form an infinite network as shown below :


3

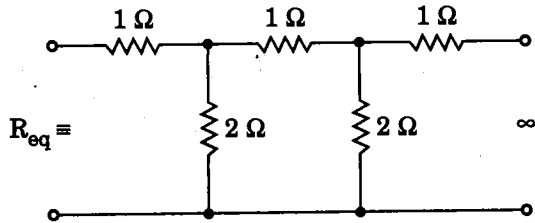

Determine the equivalent resistance,  $R_{eq}$ .


- (iii) Use KVL to determine the current,  $i$ , in the following circuit :

2

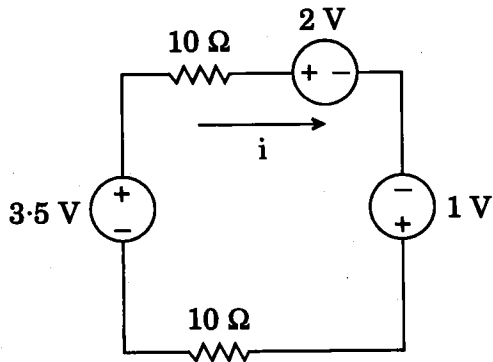


2. (a) In the circuit shown below, determine the power absorbed by  $5\text{ A}$  current source :

7

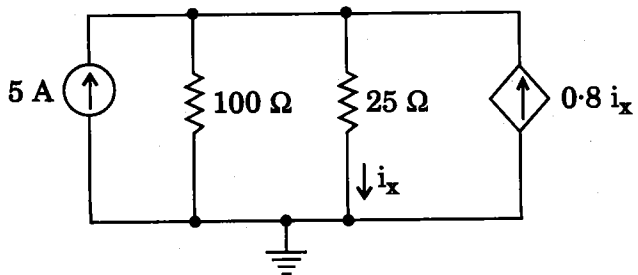

- (b) Determine the voltage  $v$  in the following circuit :


7

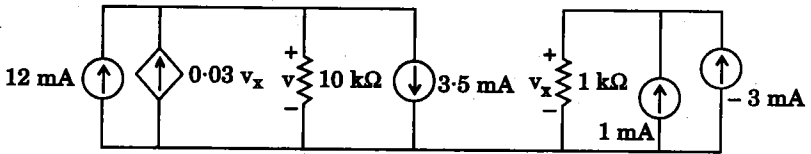

3. (a) (i) Give reason for defining a supermesh during mesh method of circuit analysis.
- (ii) Determine the power supplied to the 2.2 V source using supermesh concept.


2

5

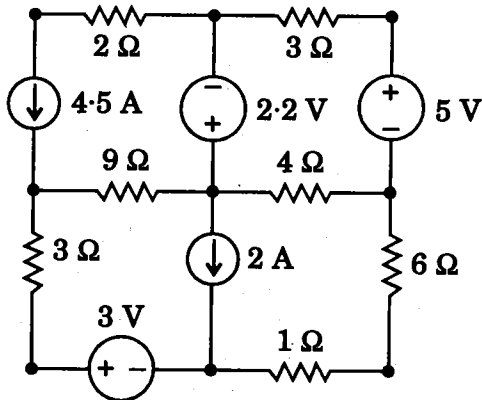


- (b) Determine the current  $i_x$  in the following circuit :


7

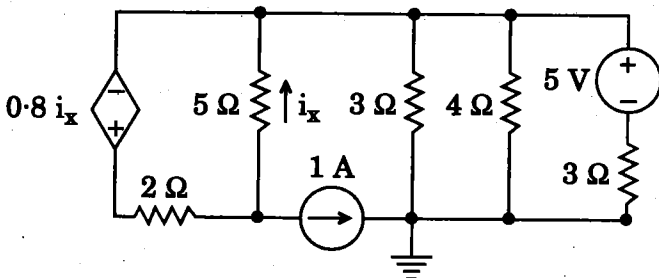

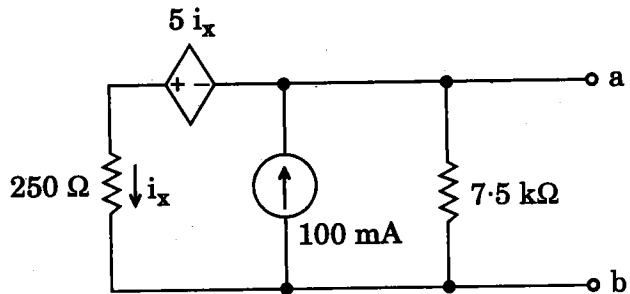
4. (a) (i) Using circuit diagrams, explain how source transformation takes place from Thevenin's equivalent circuit to Norton's equivalent circuit. 4
- (ii) Explain how Thevenin's equivalent resistance is determined in a circuit having only dependent sources. 3
- (b) Determine Thevenin's and Norton's equivalent of the following network : 7



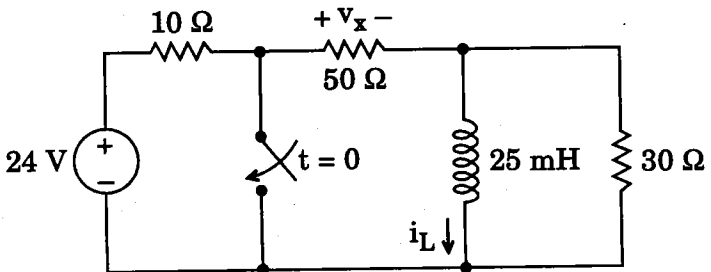
5. (a) In the following circuit, the switch is closed at time,  $t = 0$ . Determine  $v_x$  and  $i_L$  as a function of time for  $t \geq 0$ . 7



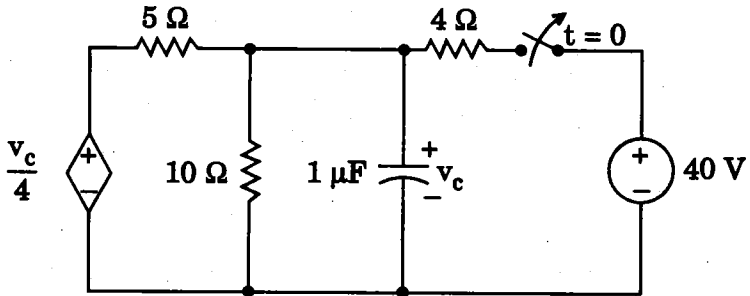- (b) In the following circuit, the switch is opened at time,  $t = 0$ . Determine  $v_c$  as a function of time. 7




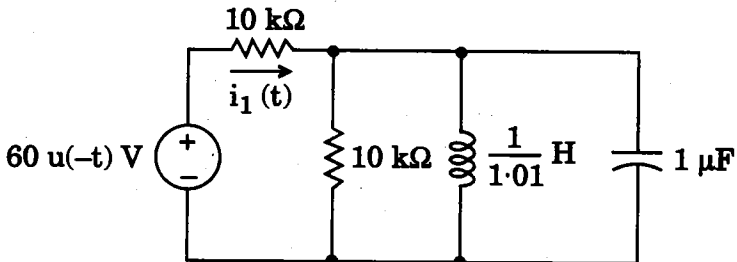6. (a) Define the following for a parallel RLC circuit :
- (i) Resonant frequency 1
  - (ii) Exponential clamping coefficient 1
  - (iii) Complex frequencies as root of characteristic equation 2
  - (iv) Overdamped condition 1
  - (v) Critical damping condition 1
  - (vi) Underdamped natural frequency 1
- (b) Determine  $i_1$  as a function of time  $t$  for  $t > 0$  in the following circuit : 7




7. (a) Determine  $R_1$  and  $R_2$  in the following circuit :

7

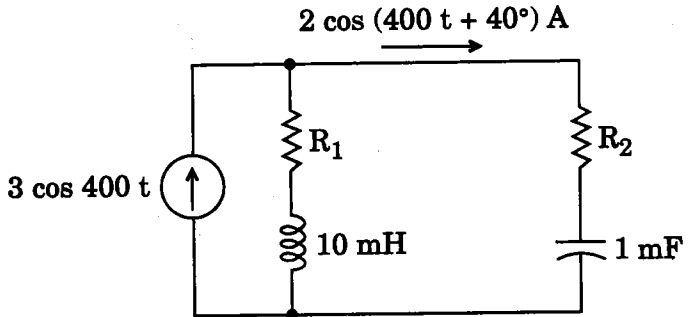

- (b) Determine the input admittance,  $Y_{in}$ , in the following circuit :


7

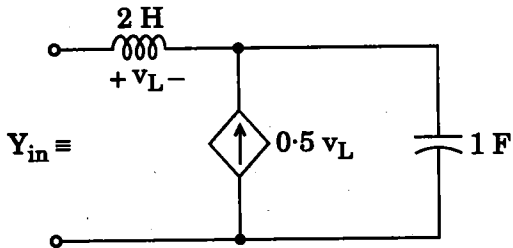

Given  $\omega = 1$  rad/sec.

8. (a) Determine the impedance to be connected across 'a - b' and the maximum power to be transferred to it in the following circuit :

7

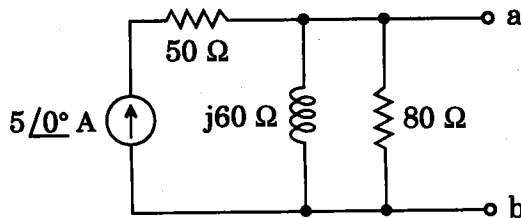

- (b) Determine the apparent power generated by the source, in the following circuit : 7

