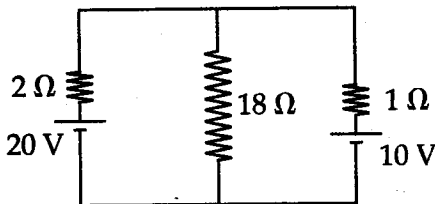


01842

**B.Tech. Civil (Construction Management) /  
B.Tech. Civil (Water Resources Engineering)****Term-End Examination****December, 2011****ET-202(B) : PRINCIPLES OF ELECTRICAL  
SCIENCES***Time : 3 hours**Maximum Marks : 70*


**Note :** Answer *any five* questions. *Symbols and abbreviations* have their usual meaning. *Use of scientific calculator is permitted.*

1. (a) Explain Thevenin's Theorem using a simple circuit. 4
- (b) A conductor of 0.7 mm diameter wire has a resistance of  $250 \Omega$ . Find the resistance of the same length of wire if its diameter is doubled. 5
- (c) Find the current in  $18 \Omega$  resistor using super position theorem in Fig. 1. 5

**Fig. 1**

2.    (a)    Explain the construction and operation of synchronous generator.    5  
      (b)    A 6 pole, 50 Hz, 400 V, three phase induction motor is operating at a slip of 2.5%. Find its actual speed and slip speed.    4  
      (c)    Describe the construction and operation of capacitor start capacitor run single phase induction motor.    5
  
3.    (a)    Discuss the load characteristics of dc shunt generator. State its applications.    5  
      (b)    Calculate the value of emf generated by a 4-pole wave wound dc generator having 40 slots with 20 conductors per slot when driven at 1200 rpm. The flux per pole is 0.016 wb.    4  
      (c)    Explain the speed control methods of dc series motor.    5
  
4.    (a)    Describe the different types of losses taking place in a transformer. The efficiency of transformer is higher than that of a motor. Why ?    5  
      (b)    State the importance and methods of safety in Electrical Installations.    4  
      (c)    Draw and discuss a typical residential wiring system.    5
  
5.    (a)    Explain the construction and operation of a typical Permanent Magnet Moving Coil (PMMC) instrument.    5

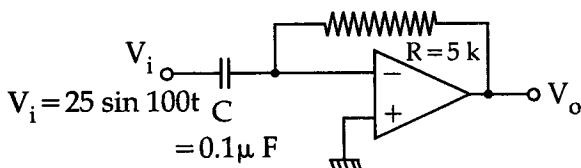- (b) Describe the circuit of OR gate and AND gate using diode. Also draw the truth table. 4
- (c) Describe the three op-amp based instrumentation amplifier. What is CMRR ? 5
6. (a) Determine the output of following circuit. 4



- (b) Design an op-amp based oscillator circuit to oscillate at a frequency of 100 kHz using inductor and capacitors. Hence find the value of resistor for  $C = 0.01 \mu F$ . 6
- (c) Explain the application of Cathode Ray Oscillator (CRO) for phase measurement. 4
7. (a) Write short notes on *any three* : 3x4=12
- Flip Flops
  - Multiplexer
  - Counters
  - Arithmetic Logic Unit
  - Interrupts
- (b) What is the clock cycle time of an 8085 microprocessor working with a crystal of 4 MHz frequency ? 2