

00852

**B.TECH. IN ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(BTECVI)**

**Term-End Examination**

**December, 2011**

**BIEL-002 : ANALOG INTEGRATED CIRCUITS  
DESIGN**


*Time : 3 hours*

*Maximum Marks : 70*

- 
- Note :** (i) *Attempt any five questions.*  
(ii) *All question carry equal marks.*  
(iii) *Assume necessary data, if required.*
- 

1. (a) Draw the basic block diagram of op-amp and explain the function of each block in detail. 7
- (b) What is current mirror ? Give name of various types of active current sources. Explain any one in detail. 7
2. (a) What is an integrator ? Draw the circuit diagram of basic integrator and derive expression for its output. 7

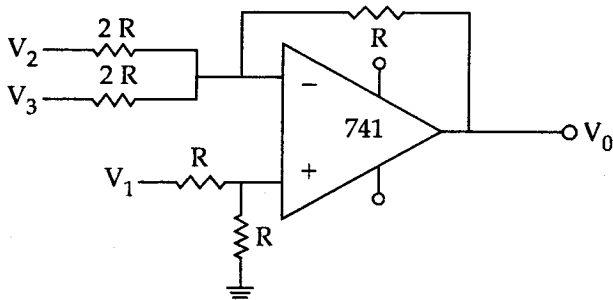- (b) Derive the expression for output voltage  $V_0$  for the given circuit. 7



3. (a) Draw the circuit diagram of sample and hold circuit and explain its operation. 7
- (b) What do you understand by precision rectifier? With the help of input and output wave forms explain the operation of full-wave precision rectifier. 7
4. (a) Explain how op-amp is used as saw-tooth wave generator. 7
- (b) What is Astable multivibrator? Draw the circuit diagram and explain its operation with help of wave forms. 7
5. (a) Design a first order low pass Butter worth filter, at cut off frequency of 1 kHz with a pass band gain of 2. 7
- (b) Explain the following for PLL : 7
- Free running frequency
  - Lock range
  - Capture range.

6. (a) With the help of circuit diagram find the expression for the output of an Anti-log Amplifier. 7
- (b) Draw the circuit diagram of I to V convertor and explain how current is converted into voltage ? 7
7. Write short notes (*Any two*) : 14
- (a) Peak detector
- (b) Schmitt Trigger
- (c) Applications of PLL
- (d) Instrumentation Amplifier.
-