

**B.Tech. ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2011

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : *Attempt any seven questions. All questions carry equal marks.*

1. (a) Simplify the Expression 2
 $[ABC(C + BD) + AB]C$
- (b) Realize XOR gate using four 2 - input 3
 NAND gates.
- (c) Design a 4 bit Gray codes to Binary codes 5
 convertor.

2. (a) Design Full Adder using two Half Adders. 5
 Use
 (i) Block Diagram of Half Adder.
 (ii) Circuit of Half Adder.
- (b) Simplify the logic function using Quine - 5
 Mcluskey method.
 $f(A, B, C, D) = \pi M(2, 7, 8, 9, 10, 12).$

3. Explain the operation of TTL as NAND gate. 10
What happens if output accidentally gets shorted to ground in :
(a) NMOS ? (b) PMOS ?
4. Design a 3-bit up/down counter with a control bit C. Use JK flip flops. 10
5. (a) Design a 4 - digit 7 - segment LED display system with leading zero blanking. 6
(b) Given the logical equation 4
 $f = ABC + \bar{A}BC + \bar{B}CD$. Simplify using K-Map.
6. (a) What is the difference between Encoders and Decoders ? 5
(b) Why Excess-3 known as self-complementing codes ? Find the excess-3 code of the following : 2+3=5
(i) 0100 (ii) 1001
7. (a) Design and explain 4-bit comparator. 5
(b) What is the difference between ROM, PROM and EPROM ? 5
8. (a) Design 32 : 1 Multiplexer using two 16 : 1 Multiplexers and one 2 : 1 Multiplexer. 5
(b) Explain Master-slave JK flip flop. 5

9. Design a digital system with two flip flops E and F and one 4-bit binary counter, A. The individual flip flops in A are denoted by A_4, A_3, A_2, A_1 , with A_4 holding the MSB of the count. A starting signal S initiates the system operation by clearing the counter A and flip flop F. The counter is then incremented by 1 starting from next clock pulse and continues to increment until operation stops. Counter bits A_3 and A_4 determine sequence of operations :

If $A_3=0$, $E \leftarrow 0$ and count continues.

If $A_3=1$, $E \leftarrow 1$ then if $A_4=0$ count continues but if $A_4=1$, $F \leftarrow 1$ on next clock pulse and system stops counting.

Draw the ASM chart of the system also.

10. Write short notes on *any two* of the following : 5x2=10

- (a) Pseudo Random Generator
 - (b) BCD Adder
 - (c) ALU
-