

**B.TECH. IN ELECTRONICS AND
COMMUNICATION ENGINEERING****Term-End Examination****December, 2011****BIEL-011 : LINEAR INTEGRATED CIRCUITS***Time : 3 hours**Maximum Marks : 70*

Note : Answer *any seven* questions. Each question carries *ten marks*. Use of scientific calculator is allowed. Q - 10 is compulsory.

1. Draw the circuit diagram of a Dual-Input balanced output differential Amplifier. 10

Following specifications are provided for a dual input balanced output differential amplifier : $V_{CC} = 10V$, $-V_{EE} = -10V$ $R_C = 2.2k\Omega$, $R_E = 4.7k\Omega$, $R_{in1} = R_{in2} = 50\Omega$, $\beta_{dc} = \beta_{ac} = 100$ and $V_{BE} = 0.715V$ typical.

- Determine I_{CQ} and V_{CEQ} values.
 - Determine the voltage gain.
 - Determine the input and output resistances, (R_{in1} , R_{in2} are source resistances)
2. Draw the basic block diagram of a typical OP-AMP. Explain the role of each block. What is the power supply requirement of an OP-AMP chip. 10

3. For the inverting Amplifier shown in FIG (3), 10
determine the maximum possible output offset
voltage due to :

- (a) Input offset voltage
- (b) Input Bias current I_B , Assume
 $V_{io}(\text{MAX}) = 6\text{mV}$, $I_B(\text{MAX}) = 500\text{nA}$.
What value of ROM is needed to reduce the
effect of I_B .

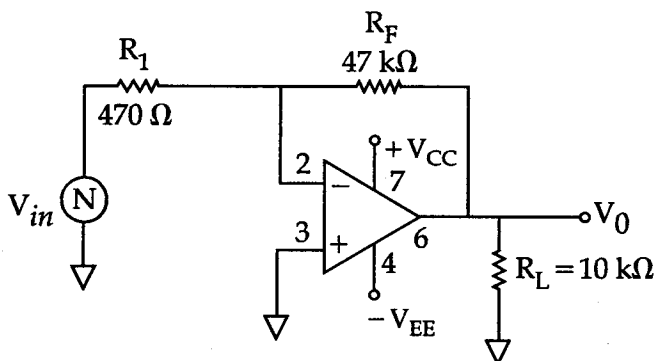


Figure - (3)

4. What is slew rate ? What are its causes ? Derive 10
a general expression for slew rate.

5. What is a Summing Amplifier ? Derive an expression for the output voltage of a summing Amplifier shown in fig (5). 10

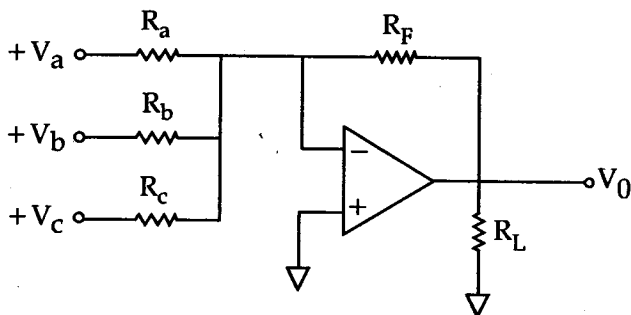


Figure - (5)

6. Draw the circuit diagram of a phase-shift oscillator using OP-AMP. Derive the necessary condition and the frequency of oscillations for the same. 10
7. Draw the circuit diagram of a sample and hold circuit using OP-AMP IC 741. Explain its operation. 10
8. Draw the circuit for a First-order high pass butterworth filter. Draw its frequency response and derive an expression for its transfer function. 10
9. What is a Current Mirror ? Draw a circuit for the same and prove that the output current is approximately equal to the input current. 10

10. Write short notes on *any two* :

2x5=10

- (a) Zero crossing detector
 - (b) CMRR
 - (c) Inverting Amplifier with feedback
-