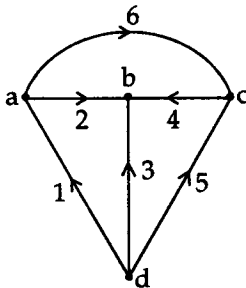


**B.TECH. - VIEP-ELECTRICAL ENGINEERING****Term-End Examination****December, 2011****BIEE-014 : NETWORK THEORY***Time : 3 hours**Maximum Marks : 70*

- Note :** (i) Attempt *any seven* Questions.  
 (ii) All questions carry *equal* marks.  
 (iii) All the questions are to be answered in English language only.

1. (a) Explain the following terms : 5x1=5
- (i) Graph
  - (ii) Tree
  - (iii) Incidence matrix with a suitable example.
  - (iv) Twings
  - (v) Oriented graph
- (b) For the graph shown in fig. (1), consider the tree formed by branches (2, 3, 4), using this tree, find out reduced incidence matrix ( $A$ ), tie - set matrix ( $B_f$ ) and cut - set matrix ( $Q_f$ ). 5

**Fig. (1)**

2. (a) In graph theory, Derive the relation among  $A$  and  $\theta_f$  where  $A$  is incidence matrix and  $\theta_f$  is fundamental cut - set matrix. 5
- (b) Explain the concept of duality with the help of fig. (2). 5

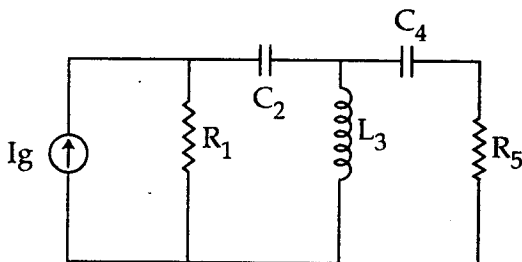


Fig. (2)

3. (a) State and prove the maximum power transfer theorem for an AC circuit. 5
- (b) Find the Thevenin's equivalent circuit for the network given in fig. (3) across A and B. 5

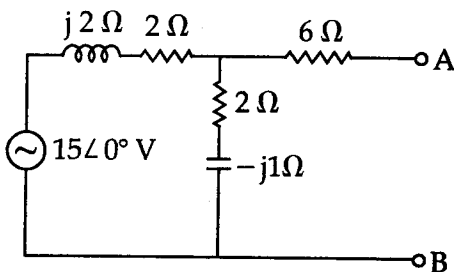


Fig. (3)

4. State super - position theorem and find the current through the  $2\Omega$  resistor using super - position theorem in fig. (4). 10

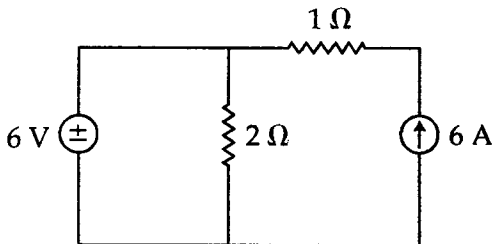


Fig. (4)

5. Enlist the necessary conditions for transfer function in terms of pole and zero locations. Draw the pole-zero diagram of the given function and obtain time domain response using it. 10

$$I(s) = \frac{4s}{(s+2)(s^2+2s+4)}$$

6. Describe the Routh Hurwitz stability criterion for stability. Determine the stability of the system whose characteristic equation is : 10

$$s^4 + 2s^3 + 3s^2 + 4s + 5 = 0$$

7. Explain in detail with figures (without proofs) the interconnection of all two port networks. 10

8. Derive the condition for reciprocity and symmetry. 10

- In term of Z parameter
- In term of T parameter

9. Synthesize the given impedance function in Foster - I and II forms. 10

$$Z(s) = \frac{8 (s^2 + 4) (s^2 + 25)}{s (s^2 + 16)}$$

10. Write short notes on *any two* of the following : 5x2=10

- (a) Active and passive filter
  - (b) Positive real function
  - (c) Image parameters
-