

**BACHELOR OF TECHNOLOGY IN  
MECHANICAL ENGINEERING  
(COMPUTER INTEGRATED  
MANUFACTURING)**

**B.Tech. (Aerospace Engineering)**

**Term-End Examination**

**December, 2011**

**01762**

**BME-021 : PRINCIPLES OF ELECTRICAL AND  
ELECTRONICS SCIENCE**

*Time : 3 hours*

*Maximum Marks : 70*

**Note :** *Answer seven questions. Question no. 1 is compulsory.  
Answer any three questions from section A and three  
from section B. Symbols and abbreviations have their  
usual meaning. Use of calculator is allowed.*

**1. State whether the following statements are  
True or False : 1x10=10**

- (a) The equivalent Resistance  $R$  of three resistances connected in parallel is given by


$$R = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3}$$

- (b) A non-linear resistor is one in which the current does not vary according to Ohm's law.

- (c) When two coils are connected such that their fluxes are in opposite direction, the equivalent inductance is given by

$$L = L_1 + L_2 + M$$

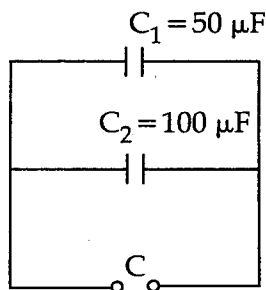- (d) The total capacitance  $C$  of the following circuit is  $150\ \mu\text{F}$ .




- (e) The rotating part of an induction motor is called armature.
- (f) There is no field circuit in a Permanent Magnet DC Motor (PMDC).
- (g) Diode and Transistor do not follow Ohm's law and are non-linear elements.
- (h) Op-amp is used as astable multivibrator.
- (i) De Morgan's First Theorem is
- $$\overline{A + B} = \overline{A} + \overline{B}$$
- (j) SR - Flip-flop is used in counters.

## SECTION-A


Answer *any three* questions from this section :

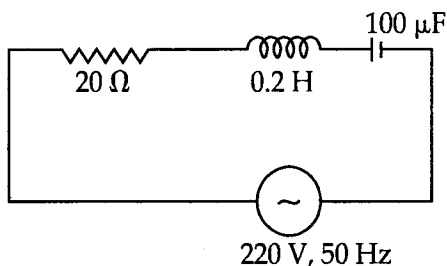2. (a) Describe the effect of temperature on resistance. 5  
 (b) A coil has a resistance of  $15\ \Omega$  when its temperature is  $20^\circ\text{C}$  and  $25\ \Omega$  when its temperature is  $60^\circ\text{C}$ . Find its temperature when the resistance is  $20\ \Omega$ . 5
  
3. (a) Develop the expression of self-inductance of a solenoid of length  $l$  metre, cross-section area  $A\ \text{m}^2$  having  $N$  turns. 5  
 (b) The steel pole piece of a permanent magnet has a cross-sectional area of  $1.6 \times 10^{-3}\ \text{m}^2$ . What is the flux density when the total flux in the pole piece is  $1.35 \times 10^{-3}\ \text{Wb}$ ? 5
  
4. (a) For the circuit shown below, calculate the power consumed in watts. 6



- (b) Why do we neglect copper losses in open circuit test of a single phase transformer? 4

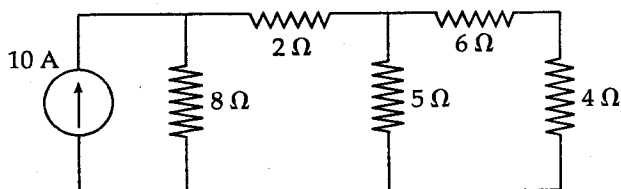5. (a) Explain the Thevenin's Theorem. 4
- (b) Calculate the current flowing through  $5\ \Omega$  resistor in circuit using Norton's Theorem. 6



6. (a) What is a transformer ? Draw its labelled diagram and write the relation between input and output voltage and number of turns. 4
- (b) A three phase squirrel cage induction motor is operating on 400V, 50Hz supply and is wound for 6 number of poles. What is the synchronous speed of rotating magnetic field in the air gap ? 6

## SECTION - B

Answer *any three* questions from this section :

- |     |      |  |   |
|-----|------|--|---|
| 7.  | (a)  | Draw the symbol and write down the characteristics of MOSFET and SCR.  | 6 |
|     | (b)  | Explain the operation of single phase half wave rectifier circuit and its waveform.                                  | 4 |
| 8.  | (a)  | Draw and explain OP Amp as an amplifier.   | 5 |
|     | (b)  | Draw the symbol and truth table of :   | 5 |
|     | (i)  | AND  |   |
|     | (ii) | OR Gate  |   |
| 9.  | (a)  | Explain with symbol and truth table the De Morgan's Theorems.  | 6 |
|     | (b)  | Discuss the concept of Tristate.   | 4 |
| 10. | (a)  | What is Flip-Flop ? Explain JK Flip-Flop with truth table.   | 5 |
|     | (b)  | Explain the operation of any one type of Shift Register.   | 5 |
| 11. | (a)  | Discuss the architecture and hardware aspects of 8085 microprocessor.  | 5 |
|     | (b)  | Discuss the difference, similarity and applications of microprocessor, microcontroller and digital signal processor. | 5 |
-