

**Diploma in Electrical and Mechanical
Engineering**

**Term-End Examination 01082
December, 2011**

BEE - 042 : ELECTRONICS

Time : 2 hours

Maximum Marks : 70

-
- Note :** (i) Question No. 1 is *compulsory*.
(ii) Attempt *any four* questions from the remaining questions numbered 2 to 8.
(iii) Use of scientific calculator is permitted.
-

-
1. (a) Select the correct answer from the given four alternatives. 7x1=7
- (i) An ideal diode is two terminal device which offers _____ resistance to current flow.
- (A) 10 ohms
(B) Zero ohm
(C) Infinite ohm
(D) 1 Ohm
- (ii) Atoms are :
- (A) 'positively charged
(B) negatively charged
(C) electrically neutral
(D) none of the above

- (iii) In a Bipolar Junction Transistor (BJT), which of the following is heavily doped ?
- (A) Collector
 - (B) Emitter
 - (C) Base
 - (D) Base and collector both.
- (iv) In cut - off region :
- (A) Emitter-base junction is forward biased and base collector junction is reverse biased.
 - (B) Emitter-base junction is reverse biased and base collector junction is forward biased.
 - (C) Emitter-base junction is forward biased and base collector junction is forward biased.
 - (D) Emitter-base junction is reverse biased and base-collector junction is reverse biased.
- (v) Unijunction transistor has :
- (A) Anode, cathode and gate
 - (B) Two bases and one emitter
 - (C) Two emitters and one base
 - (D) Source, Drain and gate.

(vi) The problem of race condition comes in :

- (A) R S Flip-Flop
- (B) J K Flip-Flop
- (C) T-Flip-Flop
- (D) None of the above

(vii) Avalanche breakdown is primarily dependent on the phenomenon of :

- (A) collision
- (B) doping
- (C) ionization
- (D) recombination

(b) Indicate *True* or *False* : 7×1=7

- (i) Passive transducers are self generating type of transducer.
- (ii) In AM, the amplitude of the carrier signal is held constant.
- (iii) In UJT, emitter is heavily doped.
- (iv) Triac is a bilateral device.
- (v) semiconductor has a negative temperature coefficient
- (vi) In Bridge rectifier peak inverse voltage is $2V_m$
- (vii) Electron in conduction band has higher energy than in valence band

2. (a) Explain the block diagram of C.R.O. 7
(b) Explain the concept of Ramp type digital voltmeter. 7
3. (a) Explain the block diagram of digital frequency meter. 7
(b) Explain the construction and applications of UJT. 7
4. (a) Define and classify the different type of transducers. 7
(b) Explain the construction and working of SCR. 7
5. (a) With the help of logic diagram. Explain the full subtractor. 7
(b) (i) Convert $(100110)_2$ into octal number 7
(ii) Convert $(2570)_{10}$ into hexadecimal number
6. (a) What is Load line and Q-point ? Explain with the help of neat and clean diagram. 7
(b) Explain the construction and working principle of NPN type Bipolar Junction Transistor (BJT). 7

7. (a) Explain the capacitor filter with full wave rectifier, draw circuit diagram and waveforms. 7
- (b) Explain ripple factor, derive mathematical expression for ripple factor of half wave and full wave rectifiers. 7
8. Write short notes on *any two* of the following : $2 \times 7 = 14$
- (a) Avalanche and zener breakdown
- (b) Intrinsic and extrinsic semiconductor
- (c) Piezoelectric transducer
- (d) Thermocouple and Thermistor.
-