

04602

DECVI/DELVI/DCSVI/ACECVI/ACELVI/ ACSVI

Term-End Examination

December, 2011

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Question No. 1 is *compulsory*.

Attempt *any five* questions.

Each question carry *equal* marks.

1. This part consists of fill in the blanks, objective and True/False type of questions.
 - (a) Only the condition $\beta A = \underline{\hspace{2cm}}$ must be satisfied for self-sustained oscillations. 2
 - (b) Full form of FET is called $\underline{\hspace{2cm}}$. 2
 - (c) Class $\underline{\hspace{2cm}}$ amplifier is normally operated in a push pull configuration in order to produce an output that is a replica of the input. 2
 - (i) AB (ii) C (iii) B (iv) A
 - (d) Negative feedback results in $\underline{\hspace{2cm}}$. 2
 - (i) decreased voltage gain
 - (ii) increased voltage gain
 - (iii) oscillation in the circuit
 - (iv) none of the above

(e) For a phase - shift oscillator, the gain of the amplifier stage must be greater than _____. 2

(i) 19 (ii) 29 (iii) 30 (iv) 1

State true or false :

(f) The efficiency of any amplifier is the ratio of signal output power to signal input power. 2

(g) In parallel resonant circuit, at resonant frequency the circuit impedance is maximum. 2

2. (a) Why class - AB amplifiers are preferred to the class - B ? Give the circuit diagrams of class - AB push pull power amplifiers. Explain the working. 7

(b) Compare FET and MOSFET mentioning the points of differences between them. Draw the cross section of a n-channel enhancement MOSFET. 7

3. (a) What is meant by figure of merit in series resonant circuit ? Plot a resonance curve for a series resonant circuit and also derive its resonance frequency. 7

- (b) Explain briefly tuned amplifier. Mention the merits of tuned amplifiers. A tank circuit uses a capacitor of 100 pF and an inductor of 15 μ H. The resistance of the inductor is 5 Ω . Determine. 7
- (i) Resonant frequency
 - (ii) Impedance at resonance
 - (iii) Q-factor
 - (iv) Bandwidth
4. (a) Discuss the advantages of negative feedback amplifiers. What do you understand by damped and undamped electrical oscillations ? 7
- (b) Explain any example of voltage series feedback with its diagram. 7
5. (a) Explain RC phase shift oscillator and its principle. Why three R - C sections are used in R - C phase shift oscillator ? 7
- (b) What do you mean by harmonic and relaxation oscillators ? Give examples of each oscillator. The parameters of a crystal oscillator equivalent circuit are given as $L_s = 0.08$ H, $C_s = 0.08$ pF, $R_s = 5$ k Ω and $C_p = 1.0$ pF. Find the resonance frequencies f_s and f_p . 7

6. (a) What is differentiator ? How is it different from integrator ? Draw their waveforms. 7
- (b) Write short notes on : 7
- (i) Clippers
- (ii) Negative resistance generator
7. (a) (i) What is a Schmitt Trigger ? Why is it called a regenerative comparator ? Define V_{UT} , V_{LT} and hysteresis in Schmitt Trigger. 7
- (ii) What is multivibrator ? Give two applications of multivibrators. Explain briefly monostable multivibrator.
- (b) What do you mean by miller sweep generator ? Discuss important steps of testing of circuits. 7
-