

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

December, 2011

01372

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

Note : Attempt any five questions. Each question carry equal marks.

1. Attempt *any two* parts : 14

(a) Discuss the significance of pole and zero in Network functions.

(b) If $f(s) = \frac{s(s+1)}{(s+4)(s^2+4s+8)}$

Find the $f(t)$ using the pole-zero diagram of the function.

(c) Discuss the necessary condition for transfer function also discuss the pole position on system stability.

- (a) Determine the voltage across the $10\ \Omega$ resistor using Nodal analysis. in fig. 1.

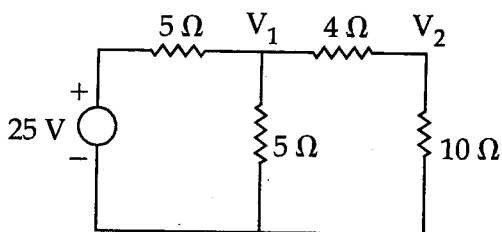


Fig. 1

- (b) Determine the current in Branch BD where galvanometer is connected in fig. 2

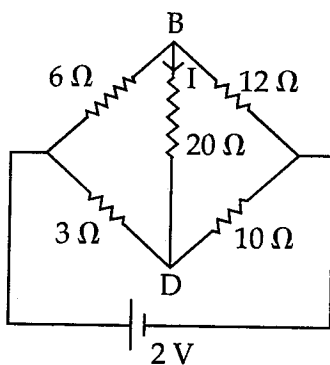


Fig. 2

- (c) Discuss the source transformations for dependent source.

3. Attempt *any two* parts :

14

- (a) Explain parallel resonance in the circuit also discuss the figure of merit.
- (b) Discuss the Natural Response of RC Network and also find the characteristic equation of RC Network.
- (c) In the circuit given in fig. 3 there is an initial voltage V_{CO} on the capacitor. The switch is closed at $t=0$. Determine the $V_C(+)$, $V_R(+)$ and $I_C(+)$ for $t \geq 0$.

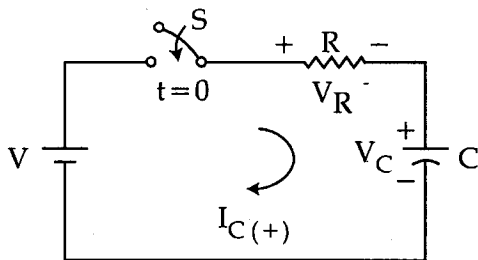


Fig. 3

4. Attempt *any two* parts :

14

- (a) Discuss the maximum power transfer theorem and prove the maximum power transferred will be $P = E^2/4R$.

- (b) Determine the current through and voltage across $30\ \Omega$ resistor using Thevenin's theorem in fig. 4.

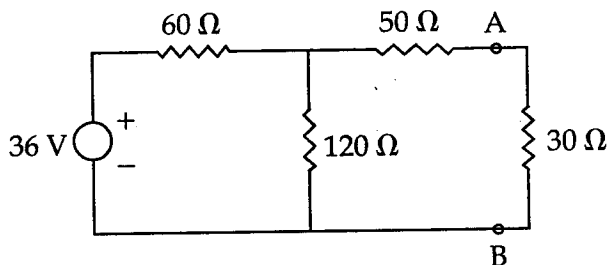


Fig. 4

- (c) Determine the current through $5\ \Omega$ resistor in the circuit using Norton's theorem in fig. 5.

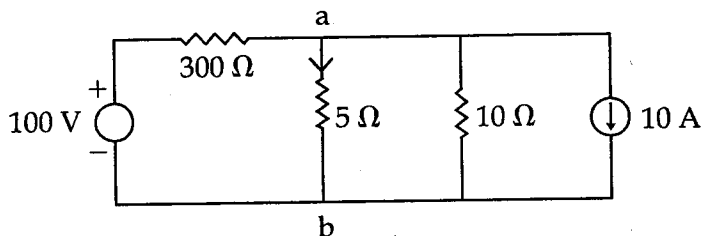


Fig. 5

5. Attempt *any two* parts :

14

- Discuss parallel - parallel interconnection in two port Network.
- Explain Impedance transformation in Resonance circuit.
- Discuss the super position theorem with example.

6. Attempt *any two* parts :

14

- (a) Find z parameter of the 2 port Network in fig. 6.

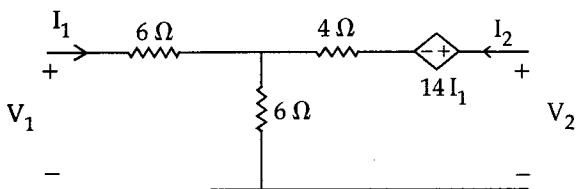


Fig. 6

- (b) Determine h parameter for the Network in fig. 7.

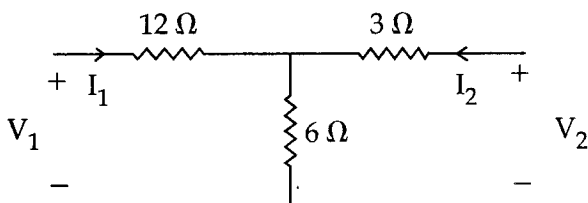


Fig. 7

- (c) Determine ABCD parameter for the Network in fig. 8.

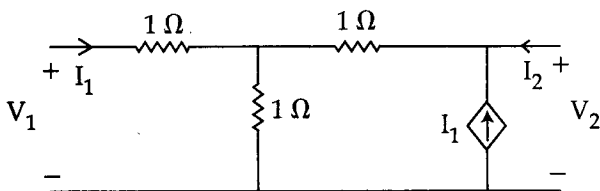


Fig. 8

7. Write short notes on *any two* :

14

- (a) π type Attenuator
 - (b) Constant K type high pass filter.
 - (c) Transmission parameter.
 - (d) Parallel resonance circuit.
-