

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

December, 2011

BIEL-030 : Digital Electronics

Time : 2 hours

Maximum Marks : 70

Note : Attempt *any five* questions and each carry *equal* marks.
Question no. *one* is *compulsory* (objective). Give the
exact answer of each question.

1. Attempt All objectives questions.

7x2=14

(a) 9^s complement of the 2368 is :

- (i) 6823 (ii) 3682
(iii) 7163 (iv) 7631

(b) TTL logic family is :

- (i) Bipolar (ii) Unipolar
(iii) Tripolar (iv) None

(c) Flip - Flop is a :

- (i) 1 bit storage device
(ii) 2 bit storage device .
(iii) 3 bit storage device.
(iv) None of them.

- (d) A full adder can be made out of :
- (i) Three half adder
 - (ii) Two half adder
 - (iii) Two half adder and or gate
 - (iv) Two half adder and an AND gate.
- (e) Boolean alzebra is essentially based on :
- (i) Symbols (ii) Logic
 - (iii) Truth (iv) None.
- (f) According to boolean alzebra $(A + \bar{A})$ equals.
- (i) A (ii) 1
 - (iii) 0 (iv) $A\bar{A}$
- (g) ECL stand for :
- (i) Emitter coupled logic.
 - (ii) End coupled logic
 - (iii) EX-OR logic
 - (iv) None of them.
2. (a) Construct a logic circüit using basic gates.
For the following expressions. 7x2=14
- (i) $x = \overline{AB(C + D)}$
 - (ii) $x = \overline{(A+B\bar{C}D\bar{E})} + \bar{B}\bar{C}\bar{D}$
- (b) Draw and explain the truth table and ckt for J-K Flip - Flop.

3. (a) What is a counter ? How it broadly classified ? Write at least two lines on each such classification. **7x2=14**
- (b) With proper ckt Diagram explain the operation of Dual slope A/D converter.
4. (a) Explain the ECL logic family and give their characteristics. **7x2=14**
- (b) Solve the following Using K-MAP.
- (i) $Y = \sum m (0,1,3,5,7,9,10,13)$
- (ii) $Y = \sum m (2,3,6,8,9,11,14,15)$
5. (a) With the suitable ckt - diagram. Explain how a four bit binary full adder works ? **7x2=14**
- (b) Explain the operation of a BCD to decimal Decoder ckt.
6. (a) Solve the following **7x2=14**
- (i) Add $(3296.32)_{12} + (9326.82)_{12}$ without changing base.
- (ii) Subtract the following usings 2^s complement.
- (A) $(1010)_2 - (0111)_2$
- (B) $(11011)_2 - (011011)_2$
- (iii) $(3258)_{10} - (9368)_{10}$ using 10^s complement.
- (b) Draw the ckt Diagram of CMOS Inverter and explain it's operation.

7. Write short notes on *any two* :

7x2=14

- (a) RAM & PROM
 - (b) Seven Segment Display System
 - (c) Shift Register.
-