

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)/ADVANCED LEVEL CERTIFICATE
COURSE IN ELECTRICAL ENGINEERING
(ACELVI)**

Term-End Examination

December, 2011

**BIEE-030 : INDUSTRIAL DRIVES AND
CONTROLS**

Time : 2 hours

Maximum Marks : 70

- Note :**
- (1) Attempt *any five* questions. All questions carry *equal* marks.
 - (2) Question no. 1 is *compulsory*. (objective type)
 - (3) Draw neat and clean Diagram if any required.

-
1. Attempt all objective type questions. **7x2=14**
- (a) To save energy during braking :
 - (i) Dynamic braking is used
 - (ii) Plugging is used
 - (iii) Regenerative braking is used
 - (iv) Mechanical braking is used.
 - (b) A/D converter is used in microprocessor control drive :
 - (i) To measure speed
 - (ii) To compute Maths equations
 - (iii) To measure voltage
 - (iv) To interface analog signal to processor.

- (c) Free wheeling Diode is used when the load is :
- (i) Inductive
 - (ii) Capacitive
 - (iii) Resistive
 - (iv) None of them.
- (d) A cycloconverter is
- (i) ac - dc converter
 - (ii) dc - ac converter
 - (iii) dc - dc converter
 - (iv) ac - ac converter
- (e) A cycloconverter can be
- (i) step down
 - (ii) step - up
 - (iii) step down or step up
 - (iv) none of them.
- (f) Thyristor can be used for control of
- (i) DC separately excited motor
 - (ii) DC shunt motor
 - (iii) DC series motor
 - (iv) All of the above
- (g) A converter with provision for both the o/p voltage and current be either positive or negative is called :
- (i) Semi converter
 - (ii) Full converter
 - (iii) Dual converter
 - (iv) Two quadrant converter.

2. (a) Explain the general principle of thyristor Drives with the help of Block Diagram. **7+7=14**
- (b) Draw and explain the circuit diagram of the single phase fully controlled converter with respect to RLE load.

3. (a) Give the working principle of three phase full converter drives. 7+7=14
- (b) Explain the regenerative braking and Rheostatic breaking mode of chopper drives.
4. (a) Give the advantages and Disadvantages of CSI and VSI fed Drives. 7+7=14
- (b) Explain the variable voltage and frequency control methods of 3ϕ induction motor.
5. (a) Analyze the operation of the chopper fed dc drive with continuous current operation. 7+7=14
- (b) How it is possible to change direction of rotation of 3ϕ induction motor using voltage controller ?
6. (a) Describe the operation of induction motor with it's equivalent ckt. 7+7=14
- (b) Explain the function of cycloconverter fed induction motor.
7. Write the short notes on *any two* : 7+7=14
- (a) Electric braking and Heating, cooling of motors
- (b) Cycloconverter principle
- (c) Difference b/w Chopper controlled and Converter controlled drives.
-