

**DECVI / DELVI / DCSVI / ACECVI /  
ACELVI / ACCSVI**

**Term-End Examination**

**December, 2011**

**OIEE-001 : BASICS OF ELECTRICAL  
ENGINEERING**

*Time : 2 hours*

*Maximum Marks : 70*

*Note:- There are seven questions. Attempt any five questions and all questions carries equal marks. Question number 1 is compulsory.*


**1. Identify True/False for (a) to (d) : 2x7=14**

- (a) An ideal current source has zero internal resistance.
- (b) Superposition theorem is applicable for linear and non-linear network.
- (c) Peak-to-peak voltage is twice the peak value of voltage.
- (d) Single phase system is more capable and reliable than 3 phase system.

**Fill in the blanks for (e) to (g) :**

- (e) Three resistors, each of R ohms are connected to form a triangle. The resistance between any two terminals will be \_\_\_\_\_  $\Omega$ .
- (f) If  $V = 200 \angle 36.9^\circ$  and  $I = 10 \angle 90^\circ$  then  $Z =$  \_\_\_\_\_.
- (g) In a 3 phase delta connection, line voltage is \_\_\_\_\_ phase voltage.

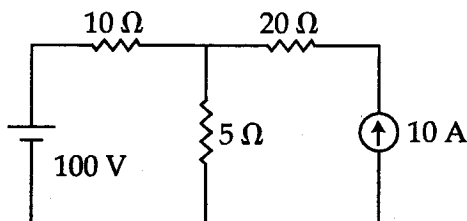2. (a) Find the current in  $5\Omega$  resistance of circuit shown using superposition theorem.  $2 \times 7 = 14$



- (b) Explain the charging methods used for lead acid battery.
3. (a) What are the advantages of AC over DC ?  
 (b) Draw and explain B-H curve.  $2 \times 7 = 14$
4. (a) Explain the concept of self induced emf and derive relation for self inductance.  $2 \times 7 = 14$   
 (b) Prove that for pure capacitive circuit power absorbed is zero.
5. (a) Define resonance. Find resonant frequency for series RLC circuit.  $2 \times 7 = 14$   
 (b) Two impedances  $Z_1 = (6 - j 0)\Omega$  and  $Z_2 = (0 - j 6)\Omega$  are connected in parallel across 100 V supply. Find :  
 (i) Current and power factor of each branch  
 (ii) Overall current and power factor.

6. (a) Derive the relationship for line current and phase current for delta connected system. **2x7=14**
- (b) A balanced star-connected load of  $(8 + j6)\Omega$  per phase is connected to a balanced 3 phase, 400V supply. Find the line current power factor, power and total volt-Amps.
7. Write short notes on *any two*. **2x7=14**
- (a) Kirchoff's Law
- (b) Lenz's Law
- (c) Faraday's Law
- (d) Thevenin's theorem.
-