

**BACHELOR OF SCIENCE (B.Sc.)****Term-End Examination**  
**June, 2011**

00938

**PHYSICS****PHE-10 : ELECTRICAL CIRCUITS AND  
ELECTRONICS***Time : 2 hours**Maximum Marks : 50*

---

*Note : Question no. 1 is compulsory. Attempt any four questions from the rest. Use of log tables and non programmable calculators is allowed. Symbols have their usual meaning.*

---

1. Attempt *any five* parts :  $2 \times 5 = 10$
- (a) State the reciprocity theorem.
  - (b) What is the role of bypass and coupling capacitors in small signal amplifier circuit ?
  - (c) Convert  $(101011.011)_2$  into its decimal equivalent.
  - (d) Draw the symbols for positive and negative edge triggered JK flip flop.
  - (e) What is the main difference between small signal and large signal amplifier ?
  - (f) Define slew rate of an op - amp and state its value for an ideal op - amp.
  - (g) State the equation for the gain of a feedback amplifier. What is its value for an oscillator ?

2. (a) Explain the variation of  $X_L$ ,  $X_C$ ,  $Z$  and phase angle with frequency for a series resonant circuit. 4

- (b) Show that in Boolean algebra 3


$$AB + A(B + C) + B(B + C) = B + AC$$

- (c) Realise OR and AND logic gate using diodes and NOT gate using transistor. 3


3. (a) Derive the expression for current gain and Input Impedance in terms of  $h$  parameters for a common emitter amplifier circuit. 4

- (b) Draw the circuit of a Colpitt's oscillator. 3+1  
Write the expression for its frequency.

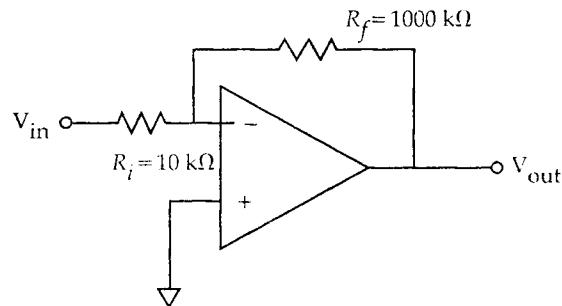- (c) Calculate voltage gain of the following 2  
circuit :



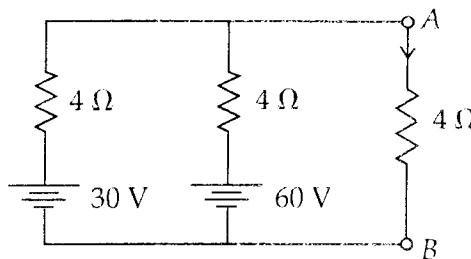4. (a) Determine the current through branch  $AB$  3  
in the following circuit :



- (b) What is meant by transistor biasing ? What is 2  
the advantage of potential divider biasing ?
- (c) Draw the circuit of basic integrator using 2+3  
op-amp. Derive the expression for its output  
voltage.
5. (a) Write the truth table for full adder and draw 3+3  
the circuit diagram of full adder using logic  
gates.
- (b) Design a  $\pi$ -type attenuator to give 40 dB 4  
attenuation and to have a characteristic  
impedance of  $100 \Omega$ .
6. (a) Draw the circuit diagram of centre-tapped 2+3  
full wave rectifier and explain its working.
- (b) Using IC LM 317, design a voltage regulator 5  
to provide 10 V output voltage.

## विज्ञान स्नातक ( बी.एस सी. )

## सत्रांत परीक्षा

जून, 2011

## भौतिक विज्ञान

## पी.एच.ई.-10 : विद्युत् परिपथ और इलेक्ट्रॉनिकी

समय : 2 घण्टे

अधिकतम अंक : 50

**नोट :** प्रश्न संख्या 1 अनिवार्य है। शेष प्रश्नों में से कोई चार प्रश्न हल करें। आप लॉग टेबल और अ-प्रोग्रामीय कैल्कुलेटर का प्रयोग कर सकते हैं। प्रतीकों के अपने सामान्य अर्थ हैं।

---

1. कोई पाँच भाग हल करें : 2×5=10

- पारस्परिकता प्रमेय का कथन लिखें।
- लघु सिग्नल प्रवर्धक में युग्मन और उपपथ संधारित्रों के क्या कार्य हैं?
- $(101011.011)_2$  को उसके दशमलव तुल्य में रूपांतरित करें।
- धनात्मक कोर और ऋणात्मक कोर ट्रिगरित JK फिलप-फ्लॉपों के प्रतीक खोचें।
- लघु सिग्नल और बृहत् सिग्नल प्रवर्धकों में मुख्य अंतर क्या है?
- आँप एम्प की दूंत घृणन दर की परिभाषा दें और आदर्श आँप-एम्प के लिए इसका मान लिखें।
- फीडबैक प्रवर्धक के लाभ का समीकरण लिखें। एक दोलित्र के लिए इस का मान क्या होता है?

2. (a) श्रेणी अनुनादी परिपथ में  $X_L$ ,  $X_C$ ,  $Z$  और कंजा कोण के आवृत्ति के साथ परिवर्तन की व्याख्या करें। 4

(b) बूलीय बीजावली में सिद्ध करें कि : 3


$$AB + A(B+C) + B(B+C) = B+AC$$

(c) डायोडों के प्रयोग से OR तथा AND और ट्रान्जिस्टर के प्रयोग से NOT गेट बनाएं। 3


3. (a) उभयनिष्ठ उत्सर्जक प्रवर्धक परिपथ के लिए धारा लाभ और निवेश प्रतिबाधा के व्यंजक  $I_o$  प्राचलों के पदों में व्युत्पन्न करें। 4

(b) कॉल्पिट दोलित्र का परिपथ चित्र खोंचें। इसकी आवृत्ति  $3+1$  का व्यंजक लिखें।

(c) निम्न परिपथ का लाभ परिकलित करें : 2

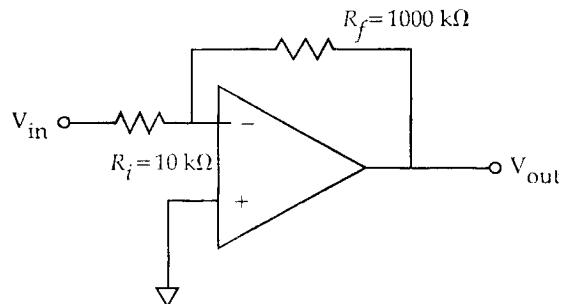

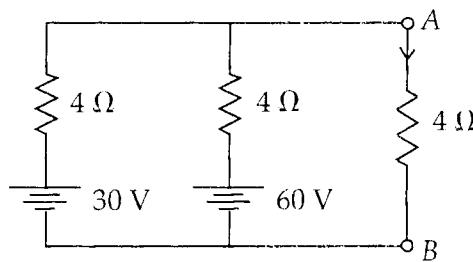4. (a) निम्न परिपथ में शाखा  $AB$  में धारा का मान परिकलित करें : 3



- (b) ट्रान्जिस्टर बायसन क्या होता है ? वोल्टता विभाजक बायसन का क्या लाभ होता है ? 2

- (c) ऑप-एम्प का प्रयोग करके बुनियादी समाकलक का परिपथ चित्र खींचे। इसकी निर्गम वोल्टता का व्यंजक व्युत्पन्न करें। 2+3

5. (a) पूर्ण योजक की सत्यमान सारणी लिखें और तर्क गेटों का प्रयोग करके पूर्ण योजक का परिपथ चित्र खींचे। 3+3

- (b) 40 dB का क्षीणन और  $100 \Omega$  की अभिलक्षणिक प्रतिबाधा प्राप्त करने के लिए एक  $\pi$ -प्रकार का क्षीणकारी डिजाइन करें। 4

6. (a) केन्द्र-अंशनिष्कासित पूर्ण तरंग दिष्टकारी का परिपथ चित्र खींचे और इसकी कार्यप्रणाली समझाएं। 2+3

- (b) IC LM 317 का प्रयोग करके 10 V की निर्गम वोल्टता हेतु वोल्टता नियंत्रक डिजाइन करें। 5