

B.Sc. (NAUTICAL SCIENCE)

Term-End Examination

December, 2013

BNA-013 : ELECTRICITY AND ELECTRONICS

Time : 2 hours

Maximum Marks : 70

-
- Note :** (i) *Non-programmable scientific calculator is allowed.*
(ii) *Attempt three questions from each section.*
(iii) *Questions No. 1 and 5 are compulsory.*
-

SECTION-A
(Electricity)

1. (a) Explain with neat sketch principle, construction and working of 3- phase Induction motor. **10**
- (b) A single-phase transformer has 525 primary turns and 70 secondary turns. If the primary is connected to a 3300 Volt supply, find the secondary voltage. Neglecting losses, what is the primary current when the secondary current is 250A ? **5**
2. (a) Define the following terms : **5**
- (i) Electric current
 - (ii) E.M.F
 - (iii) Power factor
 - (iv) Power
 - (v) Energy

- (b) Deduce the formulae when two coils are connected in series such that their fluxes are additive. 5
3. (a) Differentiate between core type and shell type transformer. 5
- (b) A moving coil voltmeter reading up to 20 milli volts has a resistance of 2 ohms. How this instrument be adopted to read voltage upto 300 Volts ? 5
4. (a) Explain the effect of temperature on resistance of pure metals, alloys and insulators. 5
- (b) Calculate the inductance of a toroid, 25cm mean diameter and 6.25 cm^2 circular cross-section wound uniformly with 1000 turns of wire. Calculate the e.m.f induced when current in it increases at the rate of 100A/second. 5

SECTION-B (Electronics)

5. (a) Explain amplitude modulation (AM). Derive the voltage equation of an AM wave. 10
- (b) Discuss steps involved in demodulation of an FM wave. Explain working of FM demodulation with the help of a circuit diagram. 5
6. (a) Describe transistor load line analysis. What is its importance? 5
- (b) In a common base connection, $\alpha = 0.95$. The voltage drop across $2 \text{ k}\Omega$ resistance which is connected in the collector is 2V. Find the base current. 5

7. (a) Derive an expression for the voltage gain of a transistor amplifier from its a.c. equivalent circuit. 5
- (b) An amplifier has an open circuit voltage gain of 1000, an input resistance of $2\text{k}\Omega$ and an output resistance of $1\text{k}\Omega$. Determine the input signal voltage required to produce an output signal current of 0.5A in 4Ω resistor connected across the output terminals. 5
8. Write short notes on **any two** of the following : 2x5=10
- (a) 7-segment display
- (b) LC tank circuit
- (c) Frequency modulation
-