

**B.Tech. Civil (Construction Management) /
B.Tech. Civil (Water Resources Engineering)**

Term-End Examination

December, 2013

**ET-202(B) : PRINCIPLES OF ELECTRICAL
SCIENCES**

Time : 3 hours

Maximum Marks : 70

Note : Answer any five questions in all. Use of calculator is permissible.

1. (a) Define resistance, inductance and capacitance. Give their V-I relationships. 6
- (b) Express the phasor's of the following sinusoidal signals in both rectangular and polar co-ordinates forms : 6
 - (i) $v(t) = 100 \sin(\omega t - 45^\circ)$
 - (ii) $v(t) = 50\sqrt{2} \cos(\omega t + 135^\circ)$
 - (iii) $i(t) = -10\sqrt{2} \sin(\omega t + 120^\circ)$
- (c) What is the advantage of an iron-cored inductor over an air-cored inductor ? 2
2. (a) Explain resonance in series RLC circuit and draw resonance curve. 6
- (b) What is KVL ? Given that $E_1 = 15V$, $E_2 = 10V$, $V_s = 20 \sin 500t$, find current I in the circuit of figure 1, 6

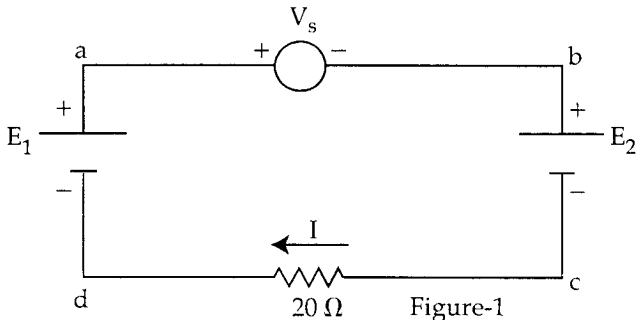


Figure-1

- (c) A practical voltage source can be converted into an equivalent current source. Draw an equivalent circuit diagram for this. 2
3. (a) What are the applications of a CRO ? 6
 (b) A 400V, 50 Hz, 3-phase voltage source supplies the following loads : 6
 (i) 10 kW at unity p.f.
 (ii) 100 kW at 0.8 p.f. lagging
 (iii) 40 kW at 0.9 p.f. lagging
 Find the overall p.f. of the load.
 (c) State and explain Norton's theorem. 2
4. (a) What are different types of flip-flops. Explain any two of them. 6
 (b) What is difference between a compiler and an assembler ? Describe ROM and RAM. 6
 (c) What is analog output voltage of a D-to-A converter corresponding to an input 1101 ? 2
5. (a) Explain the working of a dual slope integrating type ADC. 6
 (b) Explain any four applications of op-amps with relevant circuit diagrams. 6
 (c) Write a brief note on FET. 2
6. (a) How is power measured in a 3-phase circuit using two wattmeter method ? Draw the circuit diagram also. 6

- (b) A 400V, 50 Hz, 4-pole, 3 phase induction motor has the following equivalent circuit parameters at standstill = $R_1 = 2.0\Omega$, $R_2^1 = 4.0\ \Omega$, $X_1 = 2.6\ \Omega$, $X_2^1 = 2.0\ \Omega$ and $X_\phi = 70\ \Omega$. Draw equivalent circuit of the machine and find torque and power developed. 6
- (c) Write Kirchhoff's First Law. 2
7. (a) What is a multiplexer ? Draw the symbol of a 4-to-1 multiplexer showing the various inputs and outputs and write its truth table. 6
- (b) Name different types of single phase induction motors. Explain any one of them. 6
- (c) Write down the relationship between phase and line voltage, and phase and line currents for star connections in a 3-phase supply. 2
-