

**B.TECH. ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

Term-End Examination

December, 2013

BIEL-003 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

-
- Note :** (i) *Attempt any seven questions.*
(ii) *Each question carry equal marks.*
-

1. (a) What do you mean by the Gray code ? 4
What are its applications ?
- (b) Convert $(562.3)_{10}$ into octal. 2
- (c) Express -6 in 2's complement form using 8-bits. 2
- (d) Express the decimal number $(97)_{10}$ in the Excess-3 code. 2
2. (a) Simplify the following equation using Karnaugh mapping. 5
$$Y = \bar{A} \bar{D} + A \bar{B} \bar{D} + \bar{A} \bar{C} D + \bar{A} C D.$$
- (b) Convert the following expression to sum of product form. 5
$$F = (X+Y) (\bar{Y}+Z) (\bar{X}+Z).$$
3. (a) How does the look-ahead carry adder speed up the addition process ? 5
- (b) Design and implement a 4-bit binary to gray converter. 5

4. (a) Distinguish between combinational and sequential switching circuits. Give examples to each. 5
- (b) The waveforms shown in fig (i) are applied to the edge-triggered J-K flip-flop. Draw the output waveform. 5

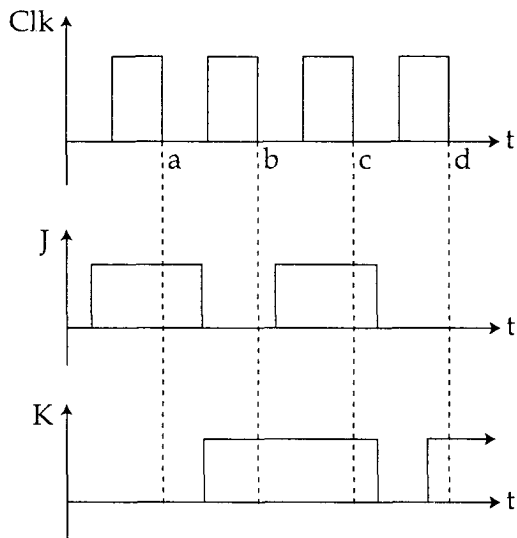


Fig. (i)

5. Design a 4-bit synchronous down counter using JK Flip flop's. Show its timing diagram. 10
6. (a) What do you mean by schottky TTL ? Why it is faster than the standard TTL ? 5
- (b) What factors limit CMOS fan-out ? 5
7. Explain random access memories of various types. 10

8. Show how an 8×1 PROM can be programmed to implement the logic function whose truth table is shown in fig (ii). 10

Truth Table

| <u>Inputs</u> | | | <u>Output</u> |
|---------------|-------|-------|---------------|
| A_2 | A_1 | A_0 | D_{out} |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Fig. (ii)

9. Describe the operation of a CMOS bilateral switch . Is there any TTL bilateral switch ? 10
10. Write short notes on any two : 2x5=10
- (a) Algorithmic state machines.
 - (b) Pseudo Random Binary sequencing generator.
 - (c) BCD adder.
-