

**B.Tech. ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2013

BIEL-011 : LINEAR INTEGRATED CIRCUITS


Time : 3 Hours

Maximum Marks : 70

-
- Note :** (i) *Attempt **any seven** questions .*
(ii) *Assume suitable data, wherever required.*
(iii) *Use of scientific calculator is **permitted**.*
-

- | | | | |
|----|-----|------------------------------------------------------------------------------------------|----|
| 1. | (a) | With the help of circuit diagram explain briefly Emitter coupled differential amplifier. | 8 |
| | (b) | Why are FET OP - amps better than BJT OP - amps ? | 2 |
| 2. | (a) | Define thermal drift , Input offset Voltage, Input offset current of an OP - amp. | 6 |
| | (b) | Discuss briefly the measurement of CMRR. | 4 |
| 3. | (a) | Explain frequency compensator techniques used in OP- amps. | 7 |
| | (b) | What is the use of a heat sink ? | 3 |
| 4. | | Define slew rate. What causes it ? How is it measured ? | 10 |

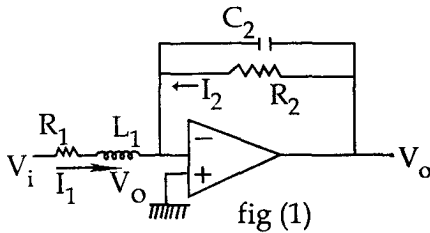5. For an op-amp shown in fig(i) Derive the transfer function. 10



6. (a) Draw and explain an OP - amp as an integrator. 7
 (b) What are the advantages of using a voltage follower amplifier? 3
7. Design a second order BPF with mid - band voltage gain $A_o = 50$, Center frequency $f_o = 160\text{Hz}$, and bandwidth = 16Hz , and $C_1 = C_2 = 0.1 \mu\text{f}$. 10
8. State the use of sample and hold circuits. Sketch the circuit arrangement along with output waveform and discuss briefly the operation of the circuit. 10
9. With neat circuit diagram explain the operation of Zero crossing detector. What is its advantages? 10
10. Write short notes on any two of the following :
 (a) Voltage limiters
 (b) Saw - tooth wave generators
 (c) Current mirror

2x5=10