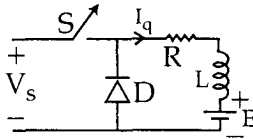


**B.Tech. ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)****Term-End Examination****December, 2013****BIEL-019 : POWER ELECTRONICS***Time : 3 hours**Maximum Marks : 70*

*Note : Attempt any five question in all. All questions carry equal marks. Missing data may be suitably assumed .
Use of calculator is permitted.*

1. (a) Draw the static V-I characteristics of SCR and explain its various modes of operation. 7
- (b) Compare power transistor, power-MOSFET and IGBT with reference to power switching applications. 7
2. (a) Explain the operation of a single phase fully controlled bridge converter feeding a highly inductive load. Draw waveforms for the output voltage, load current and source current. 10
- (b) Define di/dt and dv/dt ratings of SCR. 4
3. (a) Explain briefly the step - up chopper with neat circuit diagram. Also, write the applications of chopper. 7

- (b) The step down chopper below is operated at the switching frequency $f_s = 10$ kHz. Find the duty cycle 'k' so that average load current $I_q = 2$ A. 7



Where $V_s = 100$ V; $E = 40$ V; $L = 5$ mH; $R = 5$ Ω and diode D is an ideal diode.

4. (a) Explain the operation of a single phase full bridge inverter. Draw waveshapes for the output current when : 10
- (i) Load is purely resistive
 - (ii) Load is purely inductive
 - (iii) Load is R-L-C under damped.
- Justify the above waveshapes for different loads
- (b) What are the advantages of PWM inverters ? 4
5. (a) Give schematic diagram to implement dynamic braking and regenerative braking of d.c separately excited motor using d.c chopper and explain its working. 10
- (b) The Junction capacitance of a thyristor is 25 pF. The latching current of thyristor is 15 mA. If a capacitor of 100pF is connected across the thyristor, determine the critical dv/dt . 4

6. (a) Describe the conventional Scherbius scheme of slip energy recovery and enumerate its drawback. 10
- (b) List out the advantages of v/f control as applied to a synchronous motor. 4
7. (a) Give comparisons of DIAC and TRIAC.
- (b) What is thermal runaway of a thyristor ? How thermal runaway of a thyristor can be prevented ? $4 \times 3\frac{1}{2} = 14$
- (c) Write advantages of CSI over VSI
- (d) What is a free wheeling diode ? Write its advantages.
-