

**B.TECH. IN ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2013

**BIELE-012 : ELECTRONIC SWITCHING
CIRCUITS**

Time : 3 hours

Maximum Marks : 70

- Note :*
- (i) Attempt seven questions. All questions carry equal marks.*
 - (ii) Assume any missing data suitably.*

1. Explain the procedure for identifying the symmetric functions. Test whether or not the given switching function is symmetric 10
 $f(x, y, z) = \Sigma(1, 2, 4, 7)$.
2. Design a minimal-contact network which realizes the function. 10
 $T(w, x, y, z) = \Sigma(0, 3, 13, 14, 15)$.
3. Outline the analysis procedure for the asynchronous sequential logic circuit. Define non-critical race and explain how races can be avoided. 10
4. Explain the methods of eliminating various types of hazards and the methods for the identification of hazards. 10

5. Explain the operation of pulse-mode circuits and what are the differences between fundamental-mode and pulse-mode circuits ? 10
 6. Design a sequence detector with two asynchronous inputs. Circuit which detects a specific sequence (00, 01, 11) of combination of the two inputs. 10
 7. What is a decade counter ? Explain its operation with the help of neatly labelled circuit diagram and the state diagram. 10
 8. Explain the operation of any one type of A/D converter and any one type of D/A converter. 10
 9. Design a sequence generator whose output is a sequence 1011110. 10
 10. Explain the operation of an universal shift register obtained using D-FF. Give its circuit diagram also. 10
-