

01541

**B.Tech. ELECTRONICS
ENGINEERING - III
(BTCVI/BTECVI/BTELVI)**

Term-End Examination

December, 2013

**BIEE-001 : BASICS OF ELECTRICAL
ENGINEERING**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any five questions.

Assume missing data if any.

1. (a) Using nodal analysis find power dissipated in the 6Ω resistor. 7

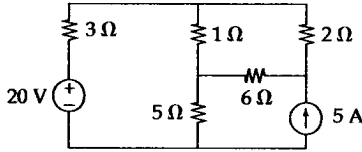


Fig. 1

- (b) Determine Thevenin's equivalent circuit across AB. 7


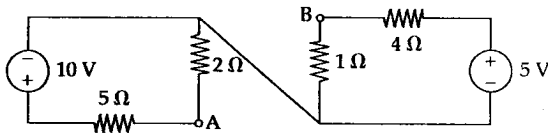


Fig. 2

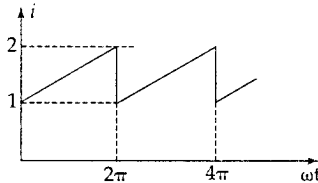2. (a) Describe the construction of Lead-acid battery. Write down the chemical equation during the charge and discharge of Lead acid battery. 7
- (b) State the indications of a fully charged Lead acid battery. 7
3. (a) Two long parallel conductors are laid at a centre to centre distance of $1.5m$ in air. Calculate and state the nature of force between them when they are carrying a current of $1000A$ each in opposite direction. Length of each conductor is $120m$. 7
- (b) Obtain an expression for energy stored in a magnetic field. 7
4. (a) Derive an expression for current at any time after switching a voltage V across R-C circuit. 7
- (b) Define and explain : 7
- (i) Co-efficient of coupling
 - (ii) Co-efficient of mutual inductance
 - (iii) Dynamically induced e.m.f.
5. (a) Calculate rms and average value of current i represented by : 7



- (b) A 0.8 Pf (Lagging) load draws $100A$ from $250V$, 1ϕ ac supply. Find : 7
- (i) The value of true power and apparent power
 - (ii) Value of circuit components

6. (a) Explain resonance in series RLC circuit and derive relation between Band width, resonance frequency and Q - factor. 7
- (b) A 15mH inductor is in series with a parallel combination of an 80Ω resistor and $20\ \mu\text{F}$ capacitor. If the angular frequency of applied voltage is $\omega = 1000\ \text{rad/sec}$ then find the admittance of the network. 7
7. (a) Derive relation between : 7
- (i) Line voltage and phase voltage
- (ii) Line current and phase current for 3 ϕ delta system
- (b) A balanced star connected load of $4 + j3\ \Omega$ per phase is connected to a balanced 3 ϕ , 400V supply. The phase current is 12A. Find Total active power, reactive power and apparent power. 7
8. Write short notes on **any two** of the following : 7x2=14
- (a) Power factor improvement.
- (b) Superposition Theorem
- (c) Charging of battery
- (d) Hysteresis and Hysteresis Loop.
-