

**DIPLOMA VIEP ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

Term-End Examination

December, 2013

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

Note : (i) Attempt five questions.

(ii) Question No. 1 is compulsory.

(iii) Use of scientific calculator is permitted.

-
1. Mention true or false for the statement given below. 7x2=14
- (a) Narrow width of the resonance curve of a circuit indicates its higher selectivity.
 - (b) Frequencies within the pass band of an ideal Bandpass filter have zero attenuation.
 - (c) Two resistors are said to be connected in series when they provide only one path for the current flow.
 - (d) Tuning circuits use the principle of resonance.
 - (e) A high -Pass filter stops low frequencies.
 - (f) With the help of poles, the stability of the network can be determined.
 - (g) Laplace transform is used to convert frequency domain signal to time domain signal.

2. (a) Determine the current through 1Ω (R_i) resistance for the circuit shown in fig (i). $2 \times 7 = 14$

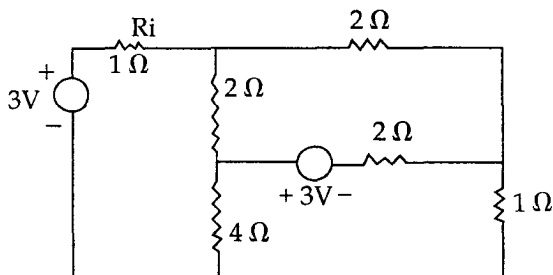


fig (i)

- (b) Find the Nortons equivalent circuit across a-b for the network shown in fig (ii).


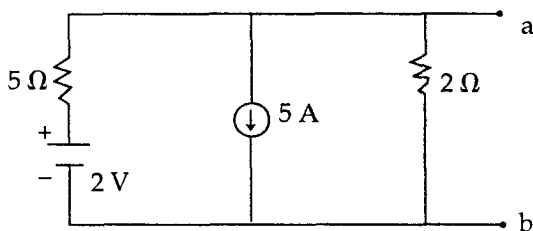


fig (ii)


3. An RLC series circuit consists of $R = 80\Omega$, $L = 40\mu$ henry and $C = 0.0783$ pf 14
 Find its (a) Resonant frequency.
 (b) Q-factor.
 (c) Bandwidth.
4. (a) Design constant - K low pass T and π sections of filter having cut off frequency 3000 Hz and nominal characteristic impedance $R_o = 600\Omega$. 2x7=14

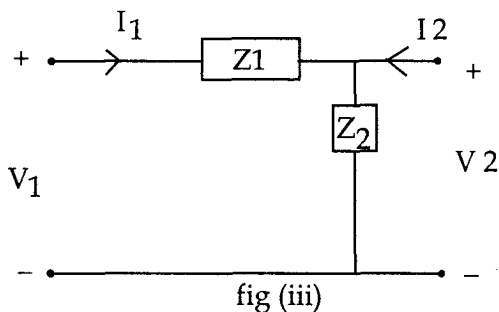- (b) The image impedances of the network shown in fig (iii) are $Z_{i1} = 100 \Omega$ and $Z_{i2} = 50 \Omega$. Calculate the Values of impedances Z_1 and Z_2 .




5. (a) Find the Z- Parameters of the network shown in fig (iv)

$2 \times 7 = 14$

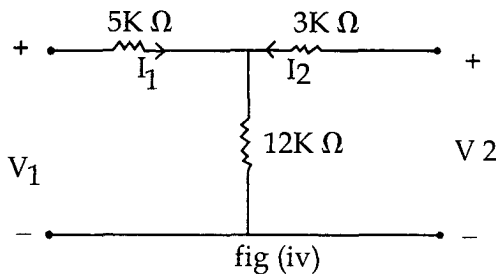

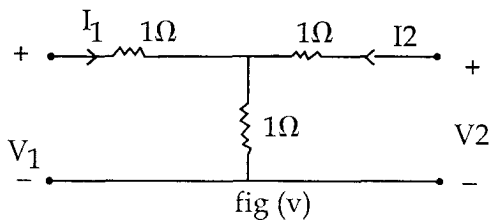- (b) Two identical sections of the network shown in fig (v) are Cascaded. Calculate the transmission Parameters (ABCD Parameters) of the resulting network .



6. (a) Discuss the Natural response of RL Series network. **2x7=14**
 (b) In the network of fig(vi), the switch is opened at $t = 0$, after having been closed for a long time, Find $i_L(t)$ for $t > 0$,

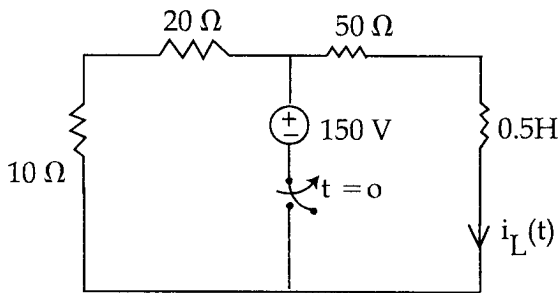


fig (vi)

7. (a) State the significance of Poles and Zeroes.
 (b) Obtain the pole zero plot of the impedance function of the network shown in fig (vii).

2x7=14

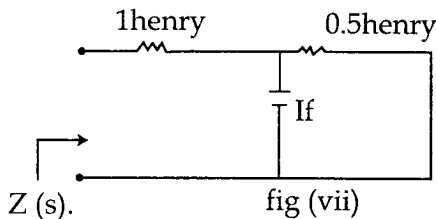


fig (vii)

8. Write short notes on *any four* : **4x3.5=14**
 (a) Attenuators
 (b) Image Impedance
 (c) Interrelation between Z-and Y- Parameters.
 (d) Parallel resonance
 (e) Constant K-type Band pass filter