

01601

**DIPLOMA IN ELECTRICAL ENGINEERING
(DELVI)/ADVANCED LEVEL CERTIFICATE
COURSE IN ELECTRICAL ENGINEERING
(ACELVI)**

Term-End Examination

December, 2013

**BIEE-030 : INDUSTRIAL DRIVES AND
CONTROLS**

Time : 2 hours

Maximum Marks : 70

-
- Note :** (i) Attempt *any five* questions.
(ii) Question No. 1 is **compulsory**. (objective types)
(iii) Draw neat and clean diagram, if any required.
-

1. (a) The minimum gate current which can turn off SCR is called : 7x2=14
- (i) Latching current
 - (ii) Holding current
 - (iii) Junction current
 - (iv) Trigger current
- (b) SCR is a :
- (i) Unilateral
 - (ii) Bilateral
 - (iii) Unijunction
 - (iv) Two Junction
- (c) Chopper has $V_o = \alpha V_s$
- (i) Step up
 - (ii) Step down
 - (iii) Both
 - (iv) None

- (d) Inverter converts :
- (i) DC to AC (ii) AC to AC
 (iii) DC to DC (iv) AC to DC
- (e) For single phase fully controlled drive connected to dc motor the expression as :

$$(i) \quad V + I_a R_a = K\phi N = \frac{2V_m}{\pi} \cos\alpha$$

$$(ii) \quad V - I_a R_a = K\phi N = \frac{V_m}{2\pi} \cos\alpha$$

$$(iii) \quad V + I_a R_a = K\phi N = \frac{V_m}{\pi} \cos\alpha$$

(iv) None

- (f) Cycloconverter converts :
- (i) AC to AC (ii) DC to AC
 (iii) AC to DC (iv) None
- (g) Triac is a :
- (i) Unidirectional
 (ii) Bidirectional
 (iii) Both
 (iv) None

2. (a) Draw and explain the working of 3 phase semi-converter drive and give advantage of variable speed drives. 7
- (b) Derive relation between firing angle and speed for dc series motor fed with single phase fully controlled rectifier. 7

3. (a) Explain single phase half wave controlled rectifier connected to a separately excited dc motor, derive relation for that. 7
- (b) Draw and explain the speed control of a 3 phase fully controlled rectifier for a dc series motor. 7
4. (a) Explain chopper fed dc drive and two quadrant and four quadrant operation of it. 7
- (b) Derive relation between voltage output and input voltage for step up and step down chopper. 7
5. (a) Derive $\alpha V_s = V_t - I_a R_a$. Where symbol has usual meaning. 7
- (b) Explain general configuration of a motor drive. 7
6. (a) Explain different method of induction motor drive. 7
- (b) Explain cyclo converter base dc drive. 7
7. (a) Explain torque - speed characteristics of 3 phase induction motor in detail. 7
- (b) Draw waveform of step up cyclo converter and fed to AC motor. 7

8. (a) Explain separately excited DC motor with single phase fully controlled converter. 7
- (b) Explain PWM control and comparison of VSI and CSI operation. 7
-