

**DIPLOMA IN ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)/
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
(ACECVI)**

Term-End Examination

December, 2012

**BIEL-029 : ELECTRONIC MEASUREMENT AND
INSTRUMENTS**

Time : 2 hours

Maximum Marks : 70

Note : (i) Attempt *any five* of the following. All questions carries *equal* marks.

(ii) Question No.1 is compulsory.

(iii) All the questions are to be answered in English language Only.

(iv) Use of scientific calculator is *permitted*.

1. Attempt the following multiple choice, Fill in the blank and *True - False (T-F)* type questions : **7x2=14**

(a) The SI unit of electric current is _____.

(b) A moving coil voltmeter has a uniform scale with 100 divisions, the Full scale reading is 200 V and 1/10 of a scale division can be estimated with a Fair degree of certainty. Determine the resolution of the instrument.

(i) 0.1 V

(ii) 0.2 V

(iii) 0.5 V

(iv) 0.8 V

- (c) The expected value of the voltage across a resistor is 80 V. However the measurement gives a value of 79 V. Then the percentage error is :
- (i) 0.25% (ii) 0.5%
 (iii) 1.25% (iv) 1%
- (d) When a.c voltage is connected to a permanent magnet moving coil, Then the :
- (i) Meter will indicate zero reading
 (ii) Meter will get damaged
 (iii) Pointer will start vibrating
 (iv) Pointer will not move at all
- (e) Digital instruments are preferred to other indicating Instruments because of better Resolution. *True/False.*
- (f) The 'Q' is defined as :
- (i) $\frac{X_L}{R}$ (ii) $\frac{X_C}{R}$
 (iii) Both (i) and (ii) (iv) None
- (g) A 1 mA meter movement with an internal resistance of 100 k Ω is to be converted into 0-100 mA ammeter. The shunt resistance required is _____.
- (i) 1.010 k Ω (ii) 0.55 k Ω
 (iii) 2 k Ω (iv) 0.25 k Ω

2. (a) Explain the term Accuracy and Precision with an example. 2x7=14
- (b) Differentiate clearly between systematic and Random errors in measurements.
3. (a) Draw a circuit of True RMS meter and explain its working. 2x7=14
- (b) Describe the working principle of Analog multimeter with a neat diagram.
4. (a) Draw the block diagram and explain the working of dual slope type DVM. 2x7=14
- (b) Draw the circuit and explain the working principle of 'Q' meter.
5. (a) Explain the working of dual trace oscilloscope with the help of Functional block diagram. 2x7=14
- (b) Explain how frequency and phase angle is measured using CRO with an example.
6. (a) Explain different types of CRO probes and its applications with examples. 2x7=14
- (b) Draw the block diagram of Spectrum Analyzer and explain.

7. (a) Draw the block diagram of RF type signal generator and explain. **2x7=14**
- (b) Explain the working principle of PMMC instrument with a neat diagram.
8. Write short notes on *any four* : **4x3.5=14**
- (a) Pulse generator
 - (b) Dead Zone
 - (c) Importance of Grounding
 - (d) DSO
 - (e) Gross error
 - (f) Ramp type DVM
-