

**DIPLOMA IN ELECTRICAL ENGINEERING  
(DELVI)**

**Term-End Examination 00651**

**December, 2012**

**BIELE-005 : INDUSTRIAL ELECTRONICS**

*Time : 2 hours*

*Maximum Marks : 70*

- 
- Note :** (i) Question no.1 is **compulsory**(objective).  
(ii) Attempt **any four** questions from rest of the questions.  
(iii) Draw neat and clean circuit diagrams if any required.
- 

1. Attempt all objective type questions : **7x2=14**
- (a) NPN transistors are preferred over PNP transistors because :
- (i) Low heat dissipation
  - (ii) Cheap and easily available
  - (iii) High mobility of holes
  - (iv) Higher mobility of electrons than holes in PNP transistors.
- (b) A power BJT is a
- (i) Voltage controlled majority carrier device.
  - (ii) Current controlled majority carrier device.
  - (iii) Current controlled minority carrier device.
  - (iv) Voltage controlled minority carrier device.

- (c) When a SCR gets turned ON, the gate drive :
  - (i) should not be removed or it will turn OFF the SCR
  - (ii) may or may not be removed
  - (iii) should be removed
  - (iv) should be removed in order to avoid increased losses and higher function temperature.
- (d) Freewheeling diode at the output of a rectifier allows :
  - (i) SCR to trigger properly
  - (ii) Turn-OFF SCR at the end of half cycle.
  - (iii) Protection of SCR against over voltage.
  - (iv) None of these
- (e) A four quadrant operations requires :
  - (i) two full converters in series
  - (ii) two full converters connected back to back.
  - (iii) two full converters connected in parallel.
  - (iv) two semi converters connected back to back.

(f) When a UJT is used for triggering of an SCR, the wave shape of the voltage obtained from UJT circuit is,

- (i) sine wave
- (ii) saw-tooth wave
- (iii) trapezoidal wave
- (iv) square wave

(g) In a three-phase half-wave rectifier the output voltage is equal to :

- (i) the most positive input phase voltage at any instant
- (ii) the difference of most positive and most negative input phases at any instant.
- (iii) the average value of the three phases
- (iv) the difference of the two positive phase voltages.

2. (a) Draw the symbols for the following : 7+7=14

- (i) SCR                      (ii) DIAC
- (iii) TRIAC                (iv) SCS
- (v) SUS                    (vi) LASCR
- (vii) IGBT

(b) Explain the two transistor analogy of an SCR.

3. (a) Describe basic structural features, working and equivalent circuit of an IGBT. 7+7=14

(b) Discuss the advantages of SCR over power BJT.

4. (a) Discuss the working of a UJT relaxation oscillator. 7+7=14
- (b) Explain various types of triggering methods of SCR.
5. (a) Give schematic representation of a 7+7=14
- (i) 3-phase half-wave rectifier circuit
- (ii) 3-phase full-wave rectifier circuit
- (iii) compare the rectification properties of the two.
- (b) Differentiate between a half controlled bridge and a fully controlled bridge.
6. (a) Explain the operation of full wave mid point converter with RL load. 7+7=14
- (b) With neat sketch, describe the function of a single phase half controlled bridge rectifier with resistive load. What will be the wave forms observed?
7. Discuss *any two* from the following : 2x7=14
- (a) Thyristor applications.
- (b) FBSOA of BJT
- (c) PUT relaxation oscillator

8. Write short notes on *any four* of the following :

**4x3.5=14**

- (a) IGBT operational characteristics
  - (b) SCR turn OFF methods
  - (c) Resistance firing circuit for SCR
  - (d) Capacitor firing circuit for SCR
  - (e) MCT's (Mos-controlled thyristor)
  - (f) RCT's (Reverse conducting thyristor)
-