

**B.Tech. DECVI/DELVI/DCSVI/ACECVI/  
ACELVI/ACCSVI****Term-End Examination****December, 2012****OIEE-001 : BASICS OF ELECTRICAL  
ENGINEERING***Time : 2 hours**Maximum Marks : 70*

---

*Note : Answer five questions in all and question number one is compulsory.*

---


1. (a) State whether the following statements are *true* or *false* : **5x1=5**
- (i) The length of the conductor or wire is doubled and its area of cross section is also doubled, then the resistance will remain unchanged.
  - (ii) M.M.F. is analogous to electric current in electric circuit.
  - (iii) The coefficient of coupling of two coils is proportional to  $\frac{1}{\sqrt{L_1 L_2}}$ .
  - (iv) The power dissipated in the pure capacitance of an R-C Series circuit will be zero.
  - (v) A 3 phase load is said to be balanced load, if all the three phases have the same impedance and power factor.

(b) Fill in the blanks for the following : 5x1=5

- (i) The unit of specific resistance is \_\_\_\_\_.
- (ii) Magnetic fuse in the magnetic circuit corresponds to \_\_\_\_\_ in electric circuit.
- (iii) The unit of Coefficient of Coupling is \_\_\_\_\_.
- (iv) In a star connected system, the phase difference between line and phase voltage is \_\_\_\_\_.
- (v) Peak factor is defined as ratio of \_\_\_\_\_ and \_\_\_\_\_.

2. (a) Explain the construction and working of a lead acid battery. 7
- (b) Explain constant current and constant voltage method of charging battery. 8

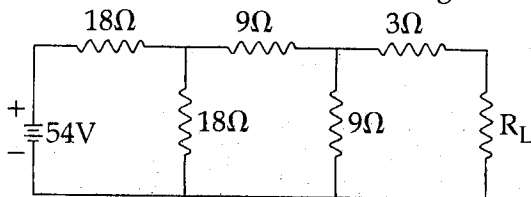3. (a) Determine the current flowing through  $R_L$  (Load Resistance) when the value of load resistance is (i)  $3\ \Omega$  (ii)  $6\ \Omega$  by using the Thevenin Theorem of the following network. 7



- (b) State and explain Kirchhoff's current and voltage laws. 8

4. (a) Explain the behaviour of a current carrying conductor when placed in the magnetic field. State Flemings left hand rule. 7
- (b) An Iron ring of mean length 1 m has an air gap of 1 mm and a winding of 200 turns. If the relative permeability of iron is 500 when a current of 1 A flows through the coil, find the flux density. 8
5. (a) State and explain Faradays law of electro-magnetic induction. 7
- (b) Two coils have a mutual Inductance of 0.6 H. If the current in one coil is varied from 4 A to 1 A in 0.2 seconds. Calculate 8
- (i) average emf induced in the other coil.
- (ii) the change of flux linking the later assuming that it is wound with 150 turns.
6. (a) Give the comparison of series and parallel resonant circuits. 7
- (b) (i) Define power factor. State its practical importance. 8
- (ii) Explain Impedance triangle, True Power and Reactive Power.

7. (a) Derive the relationship between line voltage and line current with phase voltage and phase current respectively in a star connected circuits. 7
- (b) Three coils each having resistance of  $10\ \Omega$  and inductance of  $0.02\ \text{H}$  are connected in star across  $440\ \text{V}$ ,  $50\ \text{Hz}$ , 3 phase supply. Calculate the line current and the total power consumed. 8
8. Write notes on *any two* of the following :  $7\frac{1}{2}\times 2=15$
- (a) Advantages of 3 phase over single phase system.
- (b) Ohm's law.
- (c) Care and maintenance of lead acid battery.
- (d) Difference between AC and DC.
-