

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

**00180 Term-End Examination
December, 2014**

**BIEL-002 : ANALOG AND INTEGRATED CIRCUITS
DESIGN**

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Use of scientific calculator is permitted.

1. (a) Draw a Differential Amplifier with a differential input and single ended output. Explain its working in both the cases. 5
- (b) Explain the concept of current mirror. State its application. 5

2. (a) Describe the characteristics of an ideal Op-Amp. How do the characteristics of an ideal Op-Amp differ from that of actual Op-Amp? 5
- (b) Draw the circuit diagram of an inverting amplifier using an Op-Amp. "A virtual ground exists at the input of the proper amplifier." Explain. 5

3. (a) Describe the use of an operational amplifier as an adder. What type of feedback is used in an Op-Amp adder ? Justify your answer. 5
- (b) Sketch the circuit of summer using Op-Amp to get 5
- $$V_0 = - [-V_1 + 2V_2 - 3V_3].$$
4. (a) Write a note on the use of Op-Amp as a differentiator and an integrator. 5
- (b) Draw the circuits of voltage-to-current and current-to-voltage converters using Op-Amps and explain their operations. Mention the use of these circuits. 5
5. (a) Explain the working of sample and hold circuit. 5
- (b) Draw and explain peak to peak detector circuit that gives 5
- $$V_0 = V_i (\text{max}) - V_i (\text{min}).$$
6. (a) Explain the working and construction of an Op-Amp as
- (i) a comparator
- (ii) a precision rectifier. 5
- (b) Explain how triangular waveforms are produced using Op-Amps. 5

7. (a) What is a multivibrator ? Draw the circuit diagram of an astable multivibrator and explain its operation. Show the collector voltage waveforms. 5
- (b) Explain the working of V to F and F to V converters using Op-Amps. 5
8. (a) Describe five approximations used in filter design. Use sketches as needed to show passband and stopband behaviour of the filter. 5
- (b) Give classification of filters. Explain the working of Sallen-Key low pass filter. 5
9. (a) Draw the block diagram of PLL and explain its working. Draw and explain transfer characteristics of PLL. 5
- (b) Draw the block diagram of PLL IC-565. Explain how PLL can be used in FM demodulator. 5
10. Write short notes on any *two* of the following :
- (a) Ideal (AC and DC) Op-Amp behaviour and its effect on performance 5
- (b) Saw tooth wave generators 5
- (c) Precision Rectifiers 5
-