

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00889

Term-End Examination

December, 2014

BIEL-005 : ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. Assume suitable missing data, if any. Use of scientific calculator is permitted.

1. Explain the h-parameter equivalent circuits of a transistor in CE and CC configurations with a neat diagram. 10
2. Draw the circuit diagram of Darlington amplifier. Give its main characteristics, merits and application. 10
3. A BJT is found to have $f_T = 500$ MHz, $r_{bb'} = 100 \Omega$, $g_m = 100$ m mho, $C_{b'e} = 5$ p Farad, $r_{b'e} = 900 \Omega$ and $h_{fe} = 100$ as parameters. It is used in CE amplifier with $R_S = 500 \Omega$ and $R_L = 1$ k Ω . Determine the mid-band voltage gain. 10
4. Draw the circuit of a simple Class A amplifier which can provide power amplification and explain its working. 10

5. Draw a parallel resonant circuit. Plot a curve showing the variation of circuit current. Provide a brief explanation for its variation. 10
6. In a negative feedback amplifier, $A = 100$, $\beta = 0.02$ and input signal voltage is 40 mV. Determine 10
- (i) voltage gain with feedback
 - (ii) feedback factor
 - (iii) output voltage
7. (a) Determine the oscillation frequency of a transistor based Hartley oscillator with the circuit values $L_1 = 150 \mu\text{H}$, $L_2 = 1.5 \text{ mH}$, $M = 75 \mu\text{H}$ and $C = 150 \text{ pF}$. 5
- (b) Why is Wein-bridge oscillator commonly used as an audio-oscillator? 5
8. Draw the circuit of an astable multivibrator. Justify that it is a two-stage R-C coupled amplifier using feedback. 10
9. Discuss briefly the merits and demerits of R-C coupled amplifier. 10
10. Write short notes on any *two* of the following : $2 \times 5 = 10$
- (a) Cascode amplifier
 - (b) 555 timer
 - (c) Phase shift oscillator
-