

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING**

(BTECVI)

00370

Term-End Examination

December, 2014

**BIEL-012 : ANALOG AND MIXED MODE VLSI
DESIGN**

Time : 3 hours

Maximum Marks : 70

*Note : Attempt any **seven** questions. Assume suitable missing data, if any. Use of scientific calculator is permitted.*

1. (a) Explain the operation of Sample-and-Hold Circuit.
- (b) Find the maximum sampling error for a S/H circuit that is sampling a sinusoidal input signal that could be described as

$$V_{in} = A \sin 2\pi ft, \text{ where}$$

$$A = 2 \text{ V and } f = 100 \text{ kHz}$$

Assume that the aperture uncertainty is equal to 0.5 ns. Also find the maximum resolution of an ADC which can use the above S/H circuit while maintaining a sampling error less than 1/2 LSB.

2×5=10

2. (a) What are the specifications of DAC and ADC ? Describe each.
- (b) Find the resolution of a DAC, if the output voltage is desired to change in 1 mV increments while using a reference voltage of 5 V. *2×5=10*
3. What are the mixed-signal layout issues ? Explain using suitable diagrams. *10*
4. (a) What are the various DAC architectures that exist ? Explain pipeline architecture of DAC.
- (b) Describe the Flash ADC architecture using suitable block diagram. *2×5=10*
5. Derive the expressions for the transconductance (g_m) and output resistance (r_o) of a MOSFET in the triode region. Plot these quantities and $g_m r_o$ as a function of V_{DS} , covering both triode and saturation regions. *10*
6. (a) What are the Op-amp design parameters ? Explain each.

- (b) The circuit as shown in Figure 1 is designed for a nominal gain of 10. Determine the minimum value of A_1 for a gain error of 1%.

 


Figure 1

$2 \times 5 = 10$

7. (a) What is sub-micron CMOS technology ?
How is it different from CMOS technology ?
Draw the process flow diagram of passive devices in sub-micron CMOS technology. 8
- (b) Explain the sub-micron CMOS issues during scaling. 2
8. (a) How is SNR improved in data converters ?
Explain.
- (b) Differentiate between decimating filters for ADC and interpolating filters for DAC. $2 \times 5 = 10$
9. What are the building blocks of a comparator ?
Design a basic comparator using CMOS circuits.
Explain its operation principle. 10

10. Write short notes on any *two* of the following :

2×5=10

- (a) Successive Approximation ADC
 - (b) Analog Multiplier
 - (c) Current Steering DAC
-