

**B.Tech. - VIEP - ELECTRICAL ENGINEERING
(BTELVI)**

00165

Term-End Examination

December, 2014


BIEE-017 : DIGITAL ELECTRONICS

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks. Missing data may be suitably assumed.

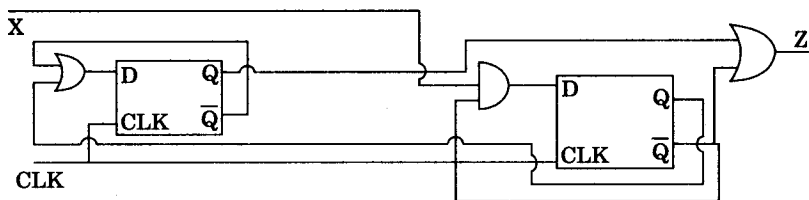1. Write the excitation equations, transition table and output table for the following clocked synchronous state machine : 10



2. Design a BCD to Excess-3 code converter using minimum number of NAND gates. 10
3. Describe and discuss the operation of a T-type flip-flop, with one application example. 10

4. (a) Draw and explain the operation of half-adder and full-adder with suitable diagram.
- (b) Explain the operation of Programmable Logic Array (PLA) with the help of suitable example. $2 \times 5 = 10$
5. What are shift registers ? Design a 4-bit ripple counter using flip-flops. 10
6. Explain 8085 Bus structure and various interrupts used in 8085. 10
7. Describe the functional block diagram of 8086 microprocessor. 10
8. Explain the following assembler directives : $5 \times 2 = 10$
- (a) ASSUME
- (b) DW
- (c) DB
- (d) END
- (e) DD
9. (a) What is the difference between 8086 and 8088 ?
- (b) Identify the contents of the Accumulator and the flag status when the following instructions are executed : $2 \times 5 = 10$
- A S Z CY
- MVI A, 7FH
- ORA A
- CPI A2H

10. What determines whether a microprocessor is considered as a 8-bit, a 16-bit or a 32-bit device ?
What are the advantages of using CPU registers for temporary data storage over using a memory location ?

10
