

DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACSVI

00630

Term-End Examination

December, 2014

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : All questions are to be answered in English Language only. Attempt any **five** questions including question no. 1 which is **compulsory**. Use of scientific calculator is permitted.

1. (a) A transformer audio amplifier is found to have an overall efficiency of nearly 70%. It is

2

(i) Class B push-pull Amplifier

(ii) Class A push-pull Amplifier

(iii) Direct Coupled Amplifier

(iv) Single-stage Class C Amplifier

- (b) Single-stage transformer coupled class A amplifier uses a transistor with maximum dissipation capability of 2.5 watts. The maximum a.c. power in the load is 2
- (i) 1.25 W
 - (ii) 2.5 W
 - (iii) 5 W
 - (iv) 0.65 W
- (c) A D-MOSFET differs from a JFET because it has no 2
- (i) Gate
 - (ii) Channel
 - (iii) Drain
 - (iv) P-N junction
- (d) State whether the following statements are *True* (T) or *False* (F). 2
- (i) The feedback ratio can be a real or complex quantity.
 - (ii) Positive feedback in an amplifier reduces the stability of gain.

(e) In R-C-phase shift oscillator

2

- (i) the β -network introduces a phase change of 180° .
- (ii) the β -network introduces a phase change of 360° .
- (iii) the amplifier gain has to be a positive number.
- (iv) $A\beta$ should be -1 .

(f) The circuit shown in Figure 1 is

2

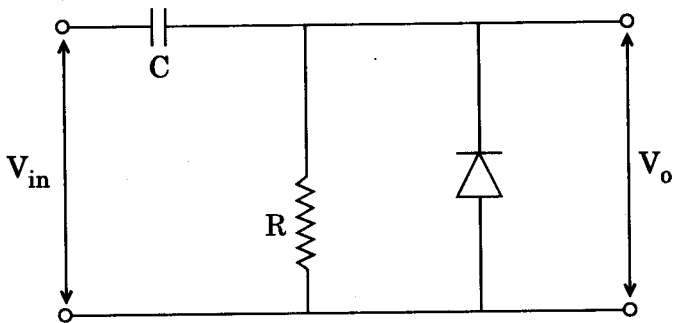


Figure 1

- (i) Positive clamper
- (ii) Negative clamper
- (iii) Differentiator
- (iv) Positive peak clipper

- (g) In Ideal bootstrap sweep shown in Figure 2
 $V = 50$ volts, $R = 1 \text{ M}\Omega$, $C = 1 \text{ }\mu\text{F}$,
 $C_1 = 100 \text{ }\mu\text{F}$. The sweep speed in volts/sec
 is

2

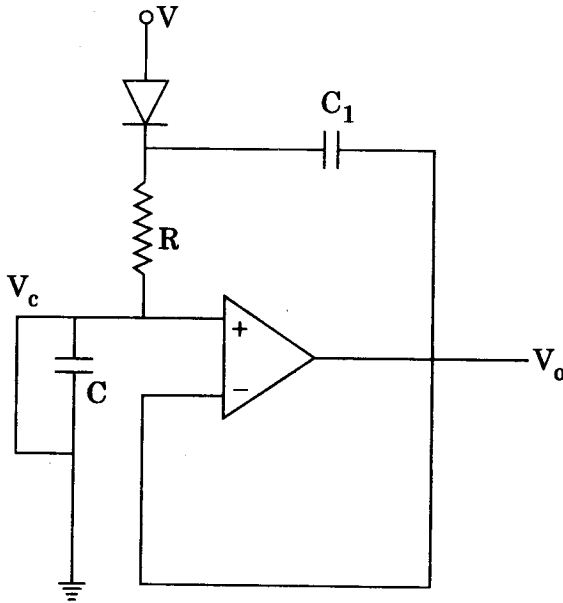


Figure 2

- (i) 50
 (ii) 0.5
 (iii) 5
 (iv) None of these
2. (a) What are the advantages of push-pull amplifiers ? Derive the expression for overall efficiency of class B push-pull amplifier.

7

- (b) A class B push-pull amplifier must deliver 10 W of audio-power to the output load. 7
- (i) If the output transformer is 80% efficient, what is the minimum power drain on the power supply under optimum conditions ?
- (ii) What is the minimum average dissipation rating required for each transistor ?
3. (a) Explain different biasing schemes used for JFET. 7
- (b) With a neat sketch describe the construction and working of an enhancement type insulated gate MOSFET using a p-type silicon bar. 7
4. (a) What is a tuned amplifier ? In which range of frequencies are tuned amplifiers used ? Draw the circuit diagram and explain the working of single-tuned amplifier. 7
- (b) Explain with the help of a diagram the working principle of a feedback amplifier. Find an expression for voltage gain with feedback. 7

5. (a) What is Barkhausen criterion ? State the basic conditions for oscillations in a feedback amplifier. What are the primary requirements to obtain steady oscillations at a fixed frequency ? 7
- (b) Explain the principle of working of Wein-Bridge oscillator circuit. Explain why negative feedback in addition to the usual positive feedback is employed in Wein-Bridge oscillators. 7
6. (a) What is a multivibrator ? Name different classes of multivibrators and briefly distinguish among them. 7
- (b) Draw the circuit of Schmitt trigger and explain its operation. 7
7. (a) Explain the working of Bootstrap and Miller sweep generators. 7
- (b) Explain the trouble-shooting of multivibrators and phase shift oscillators. 7

8. Write short notes on any **four** of the following :

$$4 \times 3 \frac{1}{2} = 14$$

- (i) Advantages of push-pull Amplifiers
- (ii) Necessity of tuned Amplifiers
- (iii) RC Integrator
- (iv) Transistor as a switch
- (v) Current Time base generator
- (vi) Trouble-shooting of clipping and clamping circuits