

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

00970

Term-End Examination

December, 2014

BIEL-028 : CIRCUITS AND NETWORKS

Time : 2 hours

Maximum Marks : 70

*Note : Attempt **five** questions. Question no. 1 is compulsory. Use of scientific calculator is permitted.*

1. Select the correct answer : $7 \times 2 = 14$

(a) How many cycles does a sine wave go through in 10 s when its frequency is 60 Hz ?

- (i) 10 cycles
- (ii) 60 cycles
- (iii) 600 cycles
- (iv) 6 cycles

- (b) A current of 100 mA through an inductive reactance of 100Ω produces a voltage drop of
- (i) 1 V
 - (ii) 6.28 V
 - (iii) 10 V
 - (iv) 100 V
- (c) While applying Thevenin's theorem, the Thevenin's voltage is equal to
- (i) short circuit voltage at the terminals
 - (ii) open circuit voltage at the terminals
 - (iii) voltage of the source
 - (iv) total voltage available in the circuit
- (d) What is the impedance of an ideal parallel resonant circuit without resistance in either branch ?
- (i) Zero
 - (ii) Inductive
 - (iii) Capacitive
 - (iv) Infinite

(e) The time constant of a series RL-circuit is

- (i) RL
- (ii) L/R
- (iii) R/L
- (iv) $e^{-R/L}$

(f) The inverse Laplace transform of $\frac{6}{s^4}$ is

- (i) 3
- (ii) t^2
- (iii) t^3
- (iv) $3t$

(g) The initial value of $x(t) = 20 - 10t - e^{25t}$ is

- (i) 20
- (ii) 19
- (iii) 10
- (iv) 25

2. (a) Determine the voltage drop across the $10\ \Omega$ resistance in the circuit shown in Figure 1.

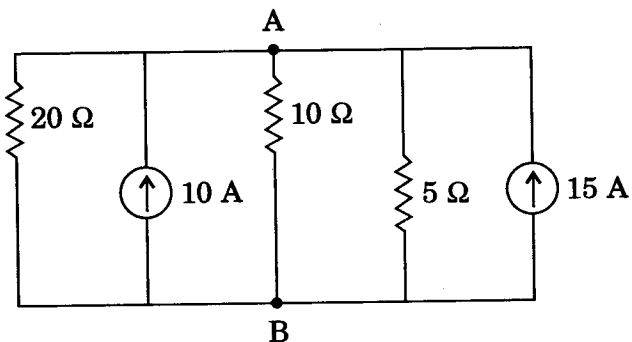


Figure 1

- (b) Find Thevenin's equivalent circuit for the circuit shown in Figure 2 across A and B. $2 \times 7 = 14$

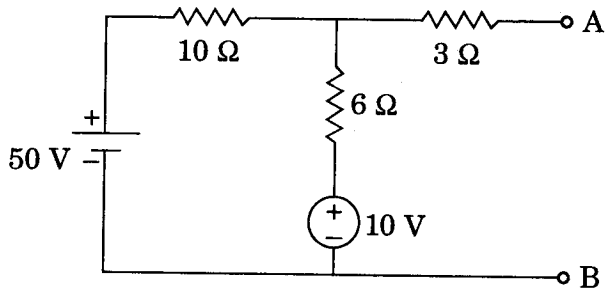


Figure 2

3. (a) Two impedances $Z_1 = (20 + j10) \Omega$ and $Z_2 = (10 - j30) \Omega$ are connected in parallel and this combination is connected in series with $Z_3 = (30 + jX)$. Find the value of 'X' which will produce resonance.
- (b) In the circuit shown in Figure 3 an inductance of 0.1 H having a Q of 5 is in parallel with a capacitor. Determine the value of capacitance and coil resistance at resonant frequency of 500 rad/sec. $2 \times 7 = 14$

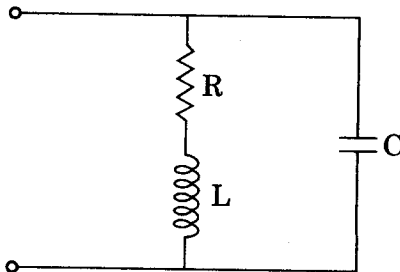


Figure 3

4. (a) A series RC circuit consists of a resistor of $10\ \Omega$ and capacitor of $0.1\ \text{F}$ as shown in Figure 4. The switch 'S' is closed at $t = 0$. Obtain the current equation. Determine the voltages across the resistor and the capacitor. (Using Classical method)

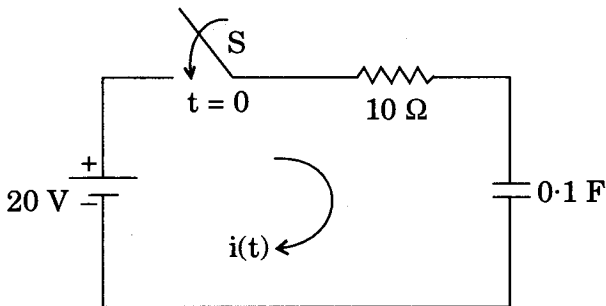


Figure 4

- (b) Determine the value of I in the given circuit in Figure 5 using Laplace transform. Assume all initial conditions to be zero. $2 \times 7 = 14$

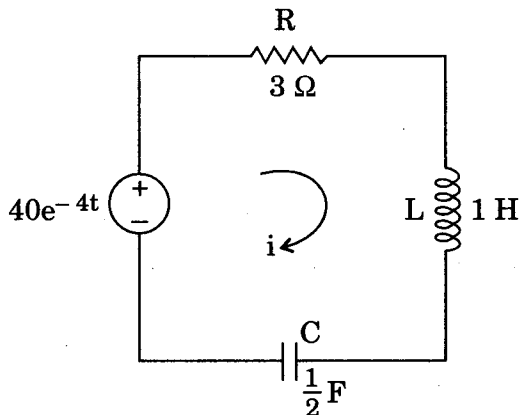


Figure 5

5. (a) Design a T-attenuator to give an attenuation of 60 dB and to work in a line of 500Ω impedance.
- (b) A T-section filter is shown in Figure 6. Calculate the value of cut-off frequency and determine the iterative impedance of the network at 1.5 kHz. $2 \times 7 = 14$

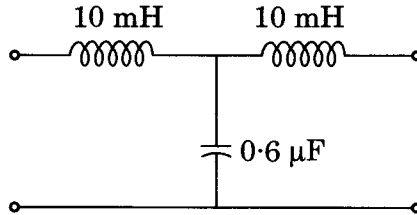


Figure 6

6. (a) For the given network function draw the pole-zero diagram and hence obtain the time-domain response $I(s) = \frac{3s}{(s+1)(s+3)}$.
- (b) For the network shown in Figure 7 obtain the transfer functions $G_{21}(s)$ and $Z_{21}(s)$ and the driving point impedance $Z_{11}(s)$. $2 \times 7 = 14$

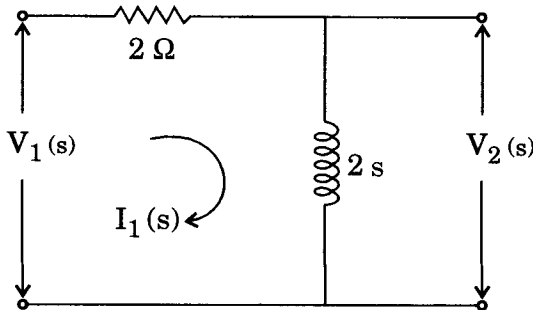


Figure 7

7. (a) Express hybrid “h” parameters in terms of “Z” (impedance) parameters.
- (b) Derive the condition for reciprocity in terms of ‘g’ parameters. $2 \times 7 = 14$
8. Write short notes on any *two* questions from each section (a) and (b) :
- (a) (i) Resonance
(ii) Step function
(iii) Source Transformation $2 \times 3 \frac{1}{2} = 7$
- (b) (i) Symmetry of two port network
(ii) Reciprocity of two port network
(iii) Superposition principle $2 \times 3 \frac{1}{2} = 7$
-