

**DIPLOMA – VIEP – ELECTRONICS AND  
COMMUNICATION ENGINEERING (DECVI) /  
ADVANCED LEVEL CERTIFICATE COURSE IN  
ELECTRONICS AND COMMUNICATION  
ENGINEERING (ACECVI)**

00436

**Term-End Examination  
December, 2014**

**BIEL-030 : DIGITAL ELECTRONICS**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt **five** questions in all. Question no. 1 is  
**compulsory.***

---

1. Choose the correct answer.

7×2=14

(a) Ones complement of the binary number  
11000101 is

- (i) 001111010
- (ii) 10111010
- (iii) 00111010
- (iv) 11000101

(b) Which of the following statements is *true* :

- (i) AND and NOT gates are necessary  
and sufficient for the realization of  
any logical function.

- (ii) OR and NOT gates are necessary and sufficient for the realization of any logical function.
  - (iii) NOR gates are sufficient to realize any logical function.
  - (iv) NAND gates are not sufficient to realize any logical function.
- (c) A multiplexer has
- (i) one data input and a number of data outputs.
  - (ii) one data output and a number of data inputs.
  - (iii) one data output, a number of data inputs and a number of select inputs.
  - (iv) one data output, a number of data inputs and a number of outputs.
- (d) A sequential circuit usually consists of
- (i) only Flip-Flops
  - (ii) Flip-Flops and gates
  - (iii) only gates
  - (iv) None of the above
- (e) A Flip-Flop is used to store
- (i) one bit of information
  - (ii) two bits of information
  - (iii) one nibble of information
  - (iv) one byte of information

- (f) Memories are used in digital systems to store
- (i) instructions
  - (ii) data
  - (iii) intermediate and final results
  - (iv) All of the above
- (g) MOS devices are used for VLSI because of
- (i) their higher propagation delay.
  - (ii) lower silicon chip area required.
  - (iii) availability of enhancement and depletion mode MOSFETs.
  - (iv) All of the above
2. (a) What do you mean by a self-complementing code ? Give examples of two self-complementing codes. 7
- (b) Convert the following decimal numbers to Gray code : 4
- (i) 12
  - (ii) 286
- (c) Convert  $(5C7)_{16}$  to decimal. 3
3. (a) State and prove De Morgan's theorem. 7
- (b) Show that both NAND gate and NOR gate are Universal gates. 7
4. (a) Explain the following terms : 7
- (i) Multiplexing
  - (ii) Demultiplexing
- (b) Design a binary full adder circuit. 7

5. (a) Explain the working of Master Slave J-K Flip-Flop and state its advantage over normal J-K Flip-Flop. 7
- (b) Design a mod-4 synchronous counter using J-K Flip-Flop. 7
6. (a) With the help of a neat diagram, explain the working of R-2R ladder network type DAC. 7
- (b) Explain Random Access Memories of various types. 7
7. (a) Define the following terms : 7
- (i) Fan-in
- (ii) Propagation delay
- (b) Discuss and draw circuit diagram for Schottky TTL NAND gate. 7
8. Write short notes on any **four** of the following :  $4 \times 3 \frac{1}{2} = 14$
- (a) DRAM
- (b) Excess-3 code
- (c) Twisted ring counter
- (d) Shift register
- (e) Sequence generator and detection
- (f) Half subtractor
-