

**DIPLOMA – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(DECVI)**

00136

**Term-End Examination
December, 2014**

BIELE-006 : ELECTRONIC PRODUCT DESIGN

Time : 2 hours

Maximum Marks : 70

Note : Attempt any **five** questions. All questions carry equal marks.

1. (a) Explain the input power consideration and protection circuit for EMI filters. 7
(b) What do you mean by regulated DC power supply ? Explain the design steps for a regulated power supply. 7
2. Describe the design steps for a lift controller using ASM technique. Explain the steps involved in implementation of the design. 14
3. (a) How is ROM classified ? Explain each classification. 7
(b) Design a 4 : 16 line decoder using 3 : 8 decoder. 7

4. What do you mean by PLD ? Draw the PAL equivalent for the following Boolean equation : 14

$$X = abcd' + a'b'c + a$$

$$Y = ab' + c'd$$

$$Z = c + ab'$$

5. (a) What do you mean by multiplexer ? Explain the difference between a decoder and a demultiplexer. 7
- (b) What do you mean by sequence detector ? Explain its working. 7
6. Design a second order high pass filter having lower cut-off frequency 1 kHz. 14
7. How is the relay interfaced with microcontroller ? Give your answer with suitable programming steps. 14
8. (a) Draw the interfacing diagram of A to D Converter using microcontroller. 7
- (b) Differentiate between Combinational and Sequential logic circuits. 7
-