

**B.Tech. – VIEP – ELECTRONICS AND
COMMUNICATION ENGINEERING
(BTECVI)**

00915 **Term-End Examination**
December, 2014

BIELE-011 : DIGITAL SYSTEM DESIGN

Time : 3 hours

Maximum Marks : 70

Note : Attempt any **seven** questions. All questions carry equal marks.

1. Design a sequential circuit with JK flip-flops to satisfy the following state equations : 10

$$A(t + 1) = A'B'CD + A'B'C + ACD + AC'D'$$

$$B(t + 1) = A'C + CD' + A'BC'$$

$$C(t + 1) = B$$

$$D(t + 1) = D'$$

2. (a) What is the difference between ROM and PROM ? Give the applications of ROM and PROM. 5
- (b) What is the difference between PAL and PLA programming structure ? 5

3. (a) Discuss the different types of faults in a digital circuit. 5
- (b) With an example, explain the principle of operation of path sensitisation method. 5
4. (a) What is the difference between 'Mealy' and 'Moore' models of sequential machine ? Explain using structural diagram. 5
- (b) A combination circuit is defined by the following functions :
- $$F_1(A, B, C) = \Sigma (3, 5, 6, 7)$$
- $$F_2(A, B, C) = \Sigma (0, 2, 4, 7)$$
- Implement the ckt with a PLA having three inputs, four product terms and two outputs. 5
5. (a) Write an application of MC 2900 in system control design. 5
- (b) Discuss the concept and features of programmable system controller. 5
6. Using MSI decoder, design MST circuits. 10
7. Write the VHDL code for a full subtractor using 10
- (a) Behavioural Modelling
- (b) Structural Modelling
8. Draw a block diagram for binary multiplier. Write a behavioural model for 4×4 binary multiplier. 10

9. Write short notes on any **two** of the following : $2 \times 5 = 10$

- (a) Races, Cycles and Hazards
 - (b) Design of testability
 - (c) Field programmable logic arrays
-