

**DIPLOMA IN ELECTRICAL
ENGINEERING (DELVI)
Term-End Examination
December, 2014**

01275

BIEE-033 : ELECTRICAL CIRCUIT THEORY

Time : 2 hours


Maximum Marks : 70

Note : Attempt any **five** questions. All questions carry equal marks. Use of scientific calculator is allowed. Assume missing data, if any.

1. (a) (i) Define Ohm's Law. 2
- (ii) A two terminal device is supplied with a variable voltage source. The across voltage and through current are measured as tabulated below :

Voltage (mV)	Current (μA)
- 4	- 6
- 2	- 3
0	2×10^{-6}
3	4.5
5	7.5

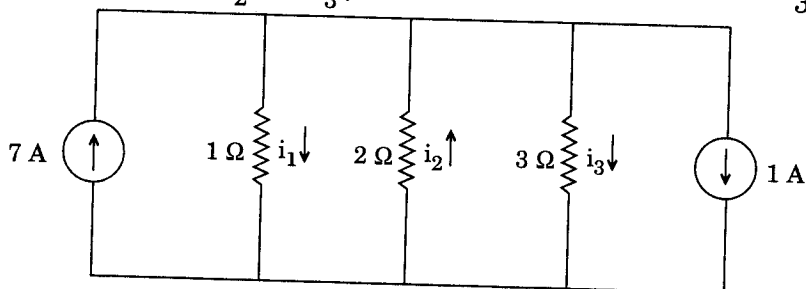
- (1) Plot the current vs voltage characteristic. 2
- (2) State with proper reason whether this device obeys Ohm's Law. 1
- (3) Compute the effective conductance and resistance of this device. 2
- (b) (i) Define Kirchhoff's Current Law and Kirchhoff's Voltage Law using mathematical expressions and diagrams. 2+2
- (ii) In the following circuit, determine i_1 , i_2 and i_3 : 3



2. (a) Draw and explain the power triangle. 7
- (b) In the circuit shown below, determine the resistance, R that will result in the
- (i) 25 kΩ resistor absorbing 2 mW of power, $3\frac{1}{2}$

- (ii) 12-V source delivering 3.6 mW to the circuit :

$3\frac{1}{2}$

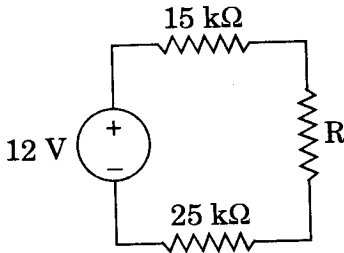


3. (a) (i) State the condition in a network analysis that requires defining a super node.


2

- (ii) In the following circuit diagram, determine the voltages, V_A and V_B w.r.t. V_E using nodal method of analysis.

5

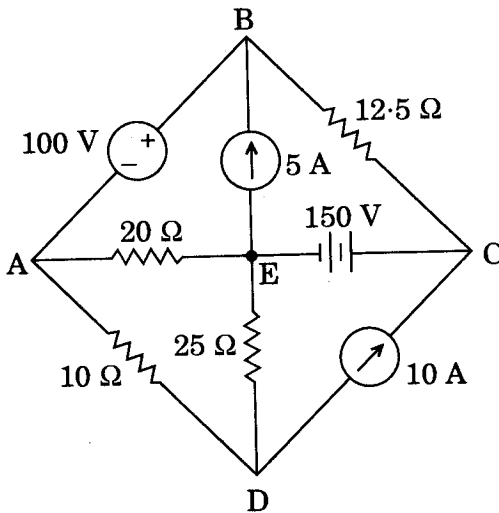

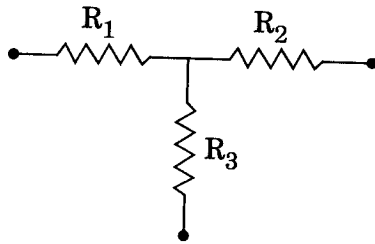- (b) (i) Given below is a star connected network.



With proper diagram, show an equivalent delta connected network. Express the resistances of Δ network in terms of R_1 , R_2 and R_3 .


2

- (ii) Define Superposition theorem.


1

- (iii) Determine the current i_x through the 20Ω resistor in the following circuit :


4

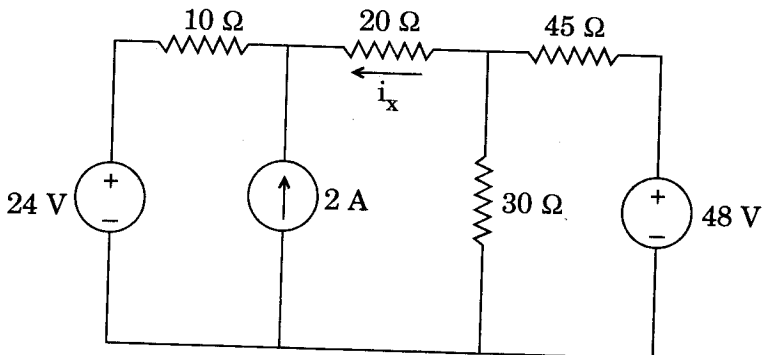

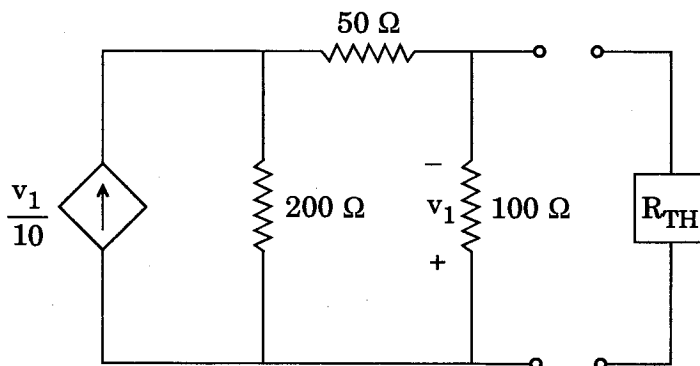4. (a) (i) With the help of diagrams, explain the transformation from a practical voltage source to a practical current source. 2
- (ii) Use source transformation to determine R_{TH} in the following circuit : 5




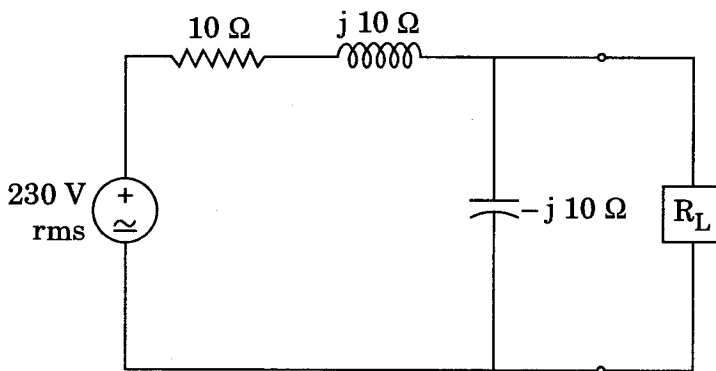- (b) (i) State Maximum power transfer theorem in terms of Thevenin's Equivalent Impedance. 2
- (ii) In the following circuit, what is the maximum average power delivered to the load if it is purely resistive ? 5



5. (a) In the following circuit, switch is closed at time, $t = 0$:

7

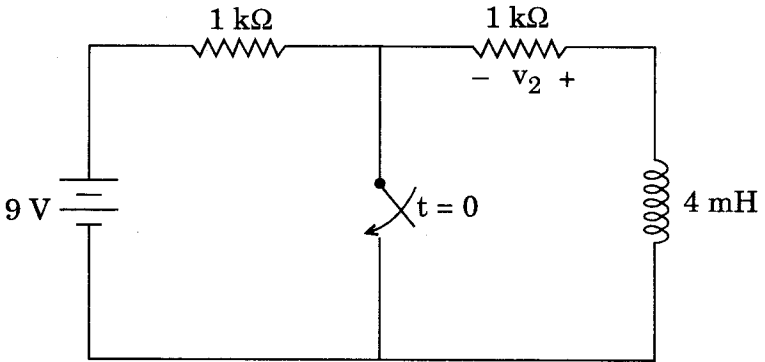

Determine the voltage v_2 at $t = 5 \mu\text{s}$.

7


- (b) Define power factor and explain the energy associated with Capacitive and Inductive circuits.

7

6. (a) Draw a source free parallel RLC circuit. Derive roots of the differential equation in terms of R, L and C.

7

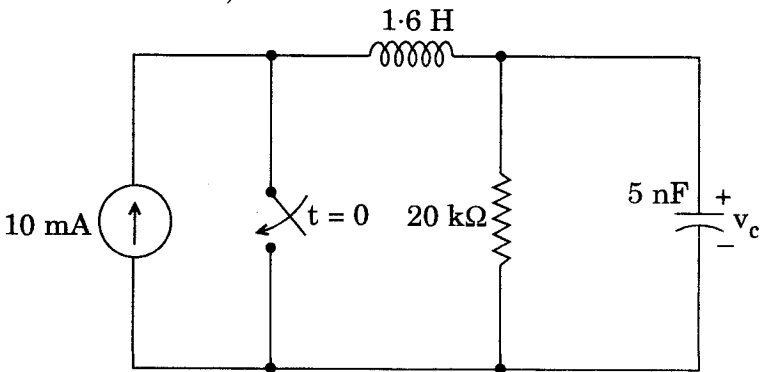
- (b) The switch in the following figure is closed at time, $t = 0$.



Determine the voltage v_c across the capacitor as a function of time.

7

7. (a) Consider the following figure :

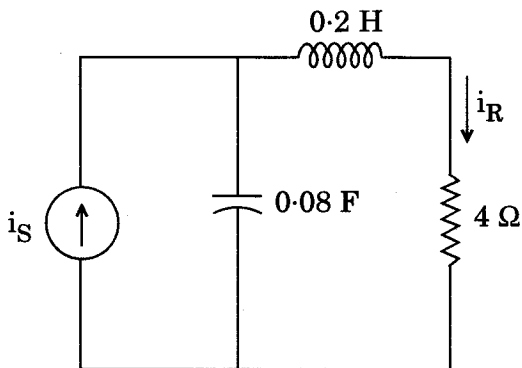

Given $i_R = 20 \angle 25^\circ$ at $\omega = 10 \text{ rad/sec}$.

Determine i_S as a complex forcing function. 7

- (b) Draw two separate phasor diagrams to represent i_R and i_S in Q. 7(a). 7

8. (a) Using circuit diagram, obtain the condition for resonance in parallel RLC circuit from fundamentals. 7

- (b) A parallel resonant circuit has $f_0 = 1 \text{ kHz}$, $Q_0 = 40$, and $|Z_{in}(j\omega_0)| = 2 \text{ k}\Omega$. Determine its Z_{in} at 1010 Hz . 7