

BTCSVI / BTECVI / BTELVI

Term-End Examination

00283

December, 2016

BIEE-001 : BASICS OF ELECTRICAL ENGINEERING


Time : 3 hours

Maximum Marks : 70

Note : Answer five questions in all. All questions carry equal marks. Use of scientific calculator is allowed.

1. (a) Discuss the effect of temperature on resistance. Mention the materials having negative temperature coefficients. What is meant by negative temperature coefficient? 7
- (b) Explain the advantages of polyphase system over single phase system. 7
2. (a) Explain the advantages and disadvantages of Lead acid battery and Nickel cadmium battery. 7
- (b) Explain the construction and working of a lead acid battery. 7

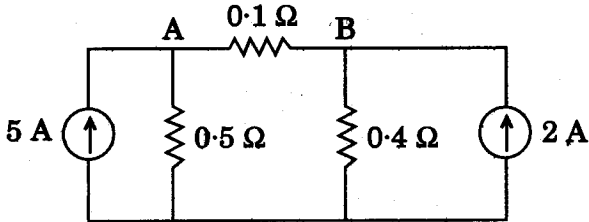3. (a) Determine the current through the 0.1Ω resistor in the following figure, using Thevenin's theorem : 7



- (b) State Kirchhoff's Current Law (KCL) and Kirchhoff's Voltage Law (KVL). 7
4. (a) Define the terms MMF, magnetic flux and magnetic reluctance and establish the relation which holds between these quantities for a magnetic circuit. 7
- (b) Estimate the number of ampere turns necessary to produce a flux of 1,00,000 lines around an iron ring of 6 cm^2 cross-section and 20 cm mean diameter having an air-gap 2 mm wide across it. Permeability of iron may be taken as 1200. Neglect the leakage flux outside the 2 mm air-gap. 7
5. (a) Write a short note on star-delta connections in a 3-phase supply and their inter-relationship. 7
- (b) Explain the Fleming's Right and Left hand rules. 7

6. (a) Explain the following terms as applied to A.C. circuits :

7

- (i) Impedance
- (ii) Power factor
- (iii) Phase angle

(b) Derive the relationship between the voltage and current for a purely capacitive circuit. Also show that the average power consumed by the circuit is zero.

7

7. Write short notes on any *two* of the following :

7+7=14

- (a) Rise and decay of current in RC circuit
- (b) Generation of 3-phase voltages
- (c) Resonance in series RLC circuit
- (d) Series and parallel connections of batteries
