

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination**

**December, 2016**

00753

**BIEE-014 : NETWORK THEORY**


*Time : 3 hours*

*Maximum Marks : 70*

**Note :**


- (i) *Attempt any seven questions.*
- (ii) *Each question carries 10 marks.*
- (iii) *Use of scientific calculator is allowed.*

1. Determine all the trees and corresponding co-trees for the graph of the network shown in Figure 1. Using the tree formed by branches (1, 2, 5), write the incidence matrix. 10

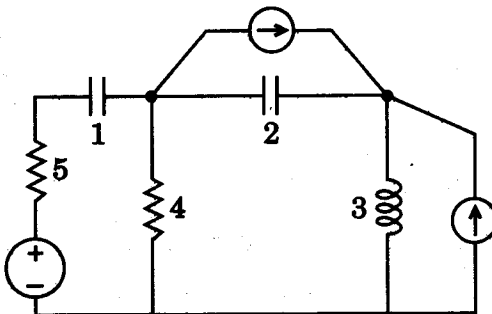


*Figure 1*

2. State maximum power transfer theorem. Derive the condition for maximum power transfer in an AC circuit. Also derive the expression for power dissipated in the load. 10
3. Given the network of Figure 2, find Norton's equivalent circuit at terminals a - b. 10

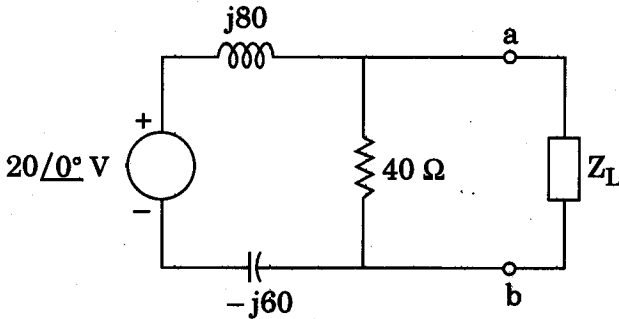

*Figure 2*

4. Determine the z and y-parameters of the network in Figure 3. 10

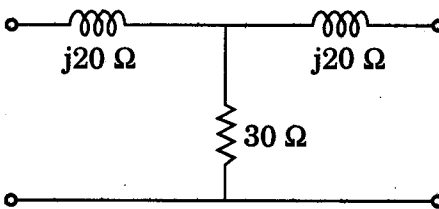

*Figure 3*

5. Explain, how a transmission line can be represented as T and  $\pi$  networks. Also enumerate T to  $\pi$  transformation. 10

6. Synthesize the first and second Cauer forms of the LC driving point impedance function

$$Z_D(s) = \frac{(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)} \quad 10$$

7. Prove that positive real functions represent physically realizable passive driving point immittances. Also explain the properties of positive real functions. 10
8. Define characteristic impedance of filter networks. Derive the expression for characteristic impedance for T-network filter. 10
9. Write short notes on any *two* of the following :  $2 \times 5 = 10$
- (a) Superposition Theorem for AC Networks
  - (b) Lattice Networks
  - (c) Active Filters
-