

**B.Tech. - VIEP - ELECTRICAL ENGINEERING  
(BTELVI)**

**Term-End Examination**

**December, 2016**

**BIEE-017 : DIGITAL ELECTRONICS**

*Time : 3 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions. All questions carry equal marks. Missing data may be suitably assumed. Use of scientific calculator is permitted.*

---

1. (a) Find the complement of  $F = wx + yz$  and then show that  $F \cdot \bar{F} = 0$  and  $F + \bar{F} = 1$ . 7
- (b) Given two eight-bit strings,  $A = 10110001$  and  $B = 10101100$ , evaluate the following : 7
  - (i) NOT A
  - (ii) NOT B
  - (iii) AND
  - (iv) OR
  - (v) XOR
2. (a) Prove that the dual of the EX-OR is also its complement. 7

- (b) Implement the following four Boolean expressions with three half adders :

7

$$D = A \oplus B \oplus C$$

$$E = \bar{A}BC + A\bar{B}C$$

$$F = AB\bar{C} + (\bar{A} + \bar{B})C$$

$$G = ABC$$

3. Define the term combinational circuit and give its simple block diagram representation. Design a combinational circuit for BCD to excess-3 code converter.

14

4. Explain the operation of a 4-bit adder/subtractor circuit with the help of a clearly labelled logic diagram and a simple mathematical example. How do the circuit defects overflow, if any exist ?

14

5. What is a Read Only Memory (ROM) ? Give a simple block diagram of a ROM. Clearly explain the working principle of a ROM with the help of an internal logic diagram of a  $32 \times 8$  ROM.

14

6. Give the architectural structure of the following :

(a) 8085 microprocessor

(b) 8086 microprocessor

What are the basic differences between the two ?

14

7. Write short notes on any *two* of the following :  $2 \times 7 = 14$

- (a) Addressing Modes of 8085
  - (b) Instruction Format of 8086
  - (c) Comparison of 8088 with 8086
-