

**DECVI / DELVI / DCSVI / ACECVI / ACELVI /
ACSVI**

00503

Term-End Examination

December, 2016

BIEL-027 : APPLIED ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : *Question number 1 is compulsory. Attempt any
four questions from the rest.*

1. This question contains objective type questions.

7×2=14

(a) Push-pull is almost always used with

- (i) Class A
- (ii) Class B
- (iii) Class C
- (iv) All of the above

- (b) The power rating of a transistor can be increased by
- (i) Raising the temperature
 - (ii) Using a heat sink
 - (iii) Using derating curve
 - (iv) Operating with no input signal
- (c) The easiest way to bias a JFET in the ohmic region is with
- (i) Voltage divider bias
 - (ii) Self bias
 - (iii) Gate bias
 - (iv) Source bias
- (d) The kind of oscillator found in an electronic wrist-watch is the
- (i) Armstrong
 - (ii) Clapp
 - (iii) Colpitts
 - (iv) Quartz crystal
- (e) With a negative feedback, the returning signal
- (i) aids the input signal
 - (ii) opposes the input signal
 - (iii) is proportional to output current
 - (iv) is proportional to differential voltage gain

- (f) A Wien bridge is sometimes called a
- (i) Notch filter
 - (ii) Twin-T oscillator
 - (iii) Phase shifter
 - (iv) Wheatstone bridge
- (g) When there is no base current in a transistor switch, the output voltage from the transistor is
- (i) Low
 - (ii) High
 - (iii) Unchanged
 - (iv) Unknown

2. (a) What are Class-C amplifiers ? How do they differ from Class-A and Class-B amplifiers ? 7
- (b) Explain why even harmonics are not present in a push-pull amplifier. Give two additional advantages of this circuit over that of a single transistor amplifier. 7
3. (a) Differentiate between the construction and applications of Enhancement type MOSFET and Depletion type MOSFET. 7

- (b) For the self-bias circuit shown below, determine the drain current I_D and gate-source voltage (V_{GS}) in Figure 3 (b). 7


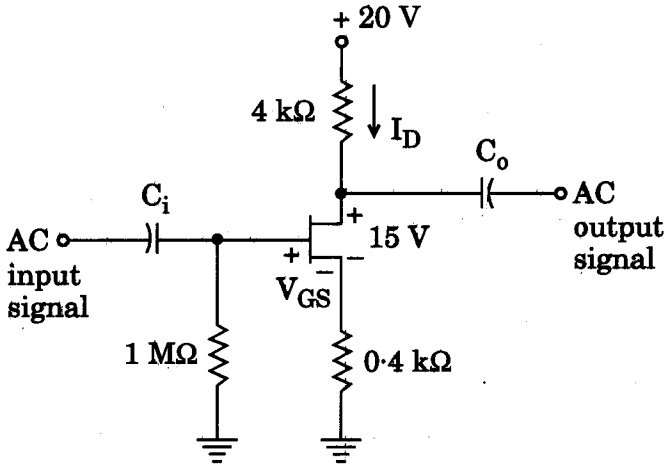


Figure 3 (b)

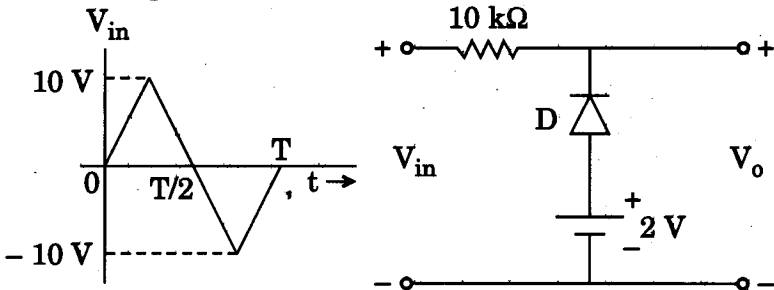4. (a) Determine and plot the V_o for the network given below : 6



- (b) With the help of a circuit diagram, briefly describe the operation of a positive clamper circuit. What is the role of resistor (R) in the clamping circuit? 8

5. (a) With the help of a circuit diagram, explain the operation of an astable multivibrator. Justify that it is a two-stage R-C coupled amplifier using feedback. 8
- (b) Draw the block diagram of feedback amplifiers in the following configurations :
- (i) Voltage series feedback
- (ii) Current series feedback
- Distinguish between voltage feedback and current feedback in an amplifier circuit, stating the merits of each. 6
6. (a) Explain the working of Colpitts oscillator. Derive an expression for the frequency of oscillation. What are the merits and demerits of this oscillator ? 7
- (b) What are the necessary conditions for sustained oscillations ? Why is loop gain in practical oscillators kept slightly greater than unity ? 7
7. (a) What is the necessity of tuned amplifiers ? Explain in brief the advantages of using a double-tuned circuit over a single-tuned circuit. 7
- (b) Explain the principles of operation of miller sweep and miller bootstrap circuits with circuit diagrams. 7

8. Write short notes on any *four* of the following :

$$4 \times 3 \frac{1}{2} = 14$$

- (a) Exponential Sweep Circuit
 - (b) RC Integrator Circuit
 - (c) Hartley Oscillator
 - (d) Schmitt Trigger and its Applications
 - (e) Different types of Negative Feedback and their Applications
 - (f) UJT Relaxation Oscillator
 - (g) Voltage Variable Resistor (VVR)
-