

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI) /
ADVANCED LEVEL CERTIFICATE COURSE IN
ELECTRONICS AND COMMUNICATION
ENGINEERING (ACECVI)**

00663

Term-End Examination

December, 2016

BIEL-030 : DIGITAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : *Attempt any five questions. Question no. 1 is compulsory. Use of scientific calculator is allowed.*

1. Choose the best answer for the following : $7 \times 2 = 14$
- (a) Convert the decimal number 221 to binary number :
- (i) 10111011
 - (ii) 11011101
 - (iii) 10111101
 - (iv) 10111100

- (b) Assign the proper odd parity bit to the code 111001.
- (i) 1111011
 - (ii) 1111001
 - (iii) 0111111
 - (iv) 0011111
- (c) Which of the following logic families has the shortest propagation delay ?
- (i) CMOS
 - (ii) BiCMOS
 - (iii) ECL
 - (iv) TTL
- (d) What is the another name for a one-shot ?
- (i) Monostable
 - (ii) Bistable
 - (iii) Astable
 - (iv) Multivibrator
- (e) The output of an OR gate with three inputs, A, B and C is low, when _____ .
- (i) $A = 0, B = 0, C = 0$
 - (ii) $A = 0, B = 0, C = 1$
 - (iii) $A = 0, B = 1, C = 1$
 - (iv) None of the above

(f) How many flip-flops are required to make a MOD-32 binary counter ?

(i) 1

(ii) 4

(iii) 6

(iv) 8

(g) A hexadecimal system has

(i) 4 bits

(ii) 8 bits

(iii) 8 bytes

(iv) None of the above

2. What is meant by TTL ? With a neat diagram, explain the operation of open collector output configuration. 14

3. Design a JK flip-flop using NOR gates and explain its operation. 14

4. Implement the expression

$$Y(A, B, C) = \Pi M(0, 2, 4, 5, 6)$$

using only NOR-NOR logic. 14

5. (a) Explain the working of carry look-ahead adder. 10

(b) Draw the circuit diagram of a 3-bit Ring counter. 4

6. (a) Given the two binary numbers $X = 1010100$ and $Y = 1000011$. Perform the subtraction $X - Y$ using 1's complement method. 7
- (b) Bring out the differences between
(i) encoder and multiplexer, and
(ii) combination and sequential logic circuits. 7
7. Write short notes on any *two* of the following: $2 \times 7 = 14$
- (a) Realization of PMOS Inverter
- (b) Shift Register
- (c) De Morgan's Theorems
-