

**B.Tech. - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (BTECVI)**

Term-End Examination

December, 2016

BIELE-004 : RF CIRCUITS

00273

Time : 3 hours

Maximum Marks : 70

Note : Attempt any seven questions. All questions carry equal marks. Missing data may be suitably assumed.

1. (a) Explain the characteristics of passive IC components at RF frequencies.
(b) What is the use of transmission lines in RF frequencies? $2 \times 5 = 10$

2. Derive the expression for input impedance of a transmission line. Also derive the expression for short and open circuit transmission line parameters. 10

3. (a) Derive an expression for the Noise Figure using a two-port network.
(b) Briefly explain the noise models that exist for active and passive components at RF frequencies. $2 \times 5 = 10$

4. Give the electrical equivalent circuit representation of the following and explain the significance of the terms appearing in the equivalent circuit : 2×5=10

- (a) High frequency capacitor
- (b) High frequency wire wound resistor

5. (a) What are the various topologies of Low Noise Amplifier ? Explain each of them briefly. 2×5=10

(b) Explain the linearity and large signal performance of LNA.

6. (a) Prove that the general expression for the amplifier efficiency (η) in terms of conduction angle (θ_0) is

$$\eta = \frac{\theta_0 - \sin \theta_0}{2 \left[\theta_0 \cos \left(\frac{\theta_0}{2} \right) - 2 \sin \left(\frac{\theta_0}{2} \right) \right]}$$

(b) What are the design parameters for high frequency amplifier design ? Explain in brief. 2×5=10

7. (a) What is a negative resistance oscillator ? Describe its working principle. 5

(b) Differentiate between an oscillator and a synthesizer. 3

(c) What is the condition of oscillation of a circuit ? 2

8. (a) What is the use of mixer ? Design a multiplier-based mixer circuit and explain its working principle.
- (b) What is the difference between sub-sampling mixers and diode-ring mixers ? 2×5=10
9. (a) Define RF power amplifiers and explain the operation of any one power amplifier with required expressions. 5
- (b) Explain the linearity considerations of RF power amplifiers. 3
- (c) Briefly explain the two-port stability criterion. 2
10. Write short notes on any *two* of the following : 2×5=10
- (a) Resonators
- (b) Neutralization and Unilateralization
- (c) S-parameters
- (d) f_T Doubler
-