

**DIPLOMA - VIEP - ELECTRONICS AND
COMMUNICATION ENGINEERING (DECVI)**

Term-End Examination

December, 2016

00563

BIELE-005 : INDUSTRIAL ELECTRONICS

Time : 2 hours

Maximum Marks : 70

Note : Answer *five* questions including question no. 1 which is **compulsory**. Missing data may be suitably assumed. Use of scientific calculator is permitted.

1. Choose the correct answer.

7×2=14

- (a) SCR is a
- (i) 5-layer 3-junction device
 - (ii) 2-layer 1-junction device
 - (iii) 4-layer 3-junction device
 - (iv) 4-layer 2-junction device
- (b) Power transistors are types of
- (i) BJTs
 - (ii) MOSFETs
 - (iii) IGBTs
 - (iv) All of the above

- (c) A GTO can be turned ON by applying
 - (i) Positive gate signal
 - (ii) Positive drain signal
 - (iii) Positive source signal
 - (iv) None of these
- (d) IGBT combines the advantages of
 - (i) BJTs and SITs
 - (ii) BJTs and MOSFETs
 - (iii) SITs and MOSFETs
 - (iv) None of these
- (e) Which semiconductor device acts like a diode and two transistors ?
 - (i) UJT
 - (ii) DIAC
 - (iii) TRIAC
 - (iv) SCR
- (f) A TRIAC is effectively
 - (i) antiparallel connection of two thyristors
 - (ii) antiparallel connection of a thyristor and a diode
 - (iii) antiparallel connection of two diodes
 - (iv) two thyristors, in parallel, to increase the current capacity of the device

- (g) Which of the following does *not* cause permanent damage to SCR ?
- (i) High current
 - (ii) High rate rise of current
 - (iii) High temperature rise
 - (iv) High rate rise of voltage
2. (a) Explain the concept of Holding and Latching current in a thyristor. 7
- (b) Draw and explain gate triggering circuit of a thyristor. 7
3. Explain the working of a single-phase full wave controlled rectifier circuit with resistive load. Draw the waveform of input-output voltages and currents. 14
4. Explain the construction of UJT with its advantages and applications. Draw the V-I characteristics with a neat sketch and discuss the region of importance. 14
5. What is commutation process ? Explain the class 'C' scheme to turn off a thyristor with a suitable circuit diagram. 14

6. With a neat sketch diagram, explain the working principle of a three-phase half wave Delta-Wye rectifier. Show the input and output voltage waveforms.

14

7. Write short notes on any *two* of the following :

2×7=14

- (a) IGBT
 - (b) Synchronized UJT Triggering
 - (c) MOS Controlled Thyristor
-