

**DIPLOMA - VIEP - ELECTRONICS AND  
COMMUNICATION ENGINEERING  
(DECVI)**

**Term-End Examination**

**December, 2016**

00473

**BIELE-006 : ELECTRONIC PRODUCT DESIGN**

*Time : 2 hours*

*Maximum Marks : 70*

---

*Note : Attempt any five questions. Each question carries equal marks. Use of scientific calculator is permitted.*

---

1. (a) Explain thermal considerations in linear regulated power supply. Write down the various applications and advantages of linear regulated power supply. 7
- (b) Describe the functions of various protection circuits like EMI filter, fuses and MCB in power supply. 7
2. (a) Define power dissipation and efficiency for the linear regulated power supply. 7
- (b) Design an FSM to detect a sequence 10110. 7

3. (a) Draw the circuit diagram of a unity gain Sallen-Key High Pass (HP) filter with its transfer function. 7
- (b) Compare Butterworth and Chebyshev filters with their transfer functions and frequency response. 7
4. (a) With the help of an example, differentiate Mealy and Moore machines. 7
- (b) Explain DAC with pulse width modulation for analog output. 7
5. (a) Explain the working of a vending machine with the help of ASM technique. 7
- (b) Design a second order Butterworth Band Pass (BP) active filter for a lower cut-off frequency of 1 kHz and a higher cut-off frequency of 2 kHz. 7
6. (a) Explain KRC filter realization techniques. 7
- (b) Draw and explain the output interfacing of Relay with microcontroller based Data Acquisition System. 7
7. (a) Explain how transducers are selected in Data Acquisition System. 7
- (b) Describe the working of front-end analog signal conditioning circuit for microcontroller. 7

8. Write short notes on any *two* of the following : 2×7=14

- (a) Fuse Map Generation
  - (b) Indicators for Over Voltage and Over Current
  - (c) P-Spice
-